


# Combinational Circuits

Logic Design
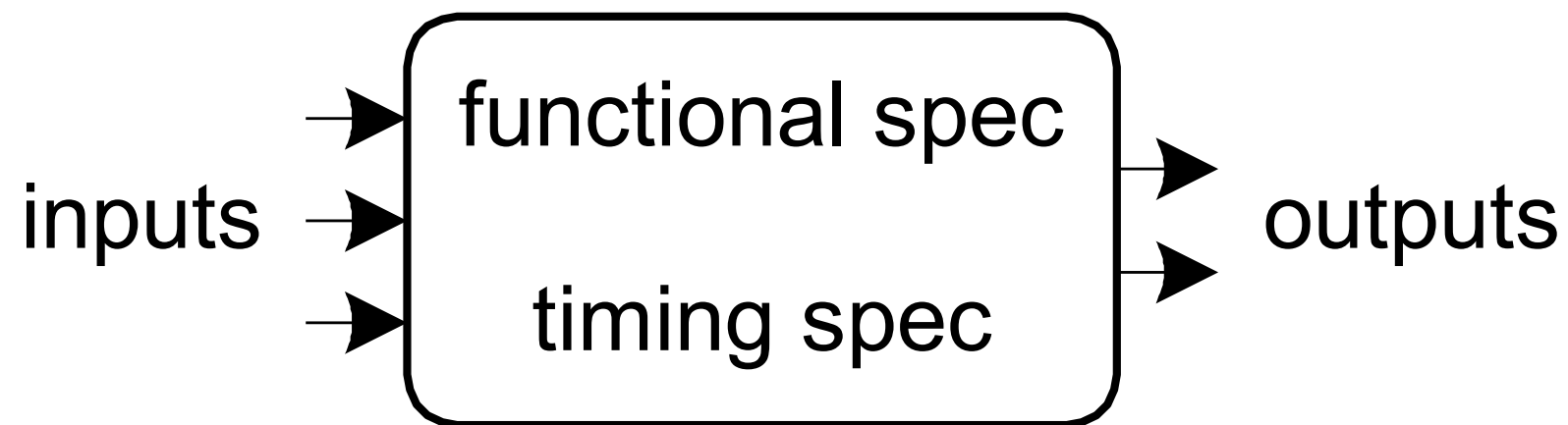
# Introduction


A logic circuit is composed of:

- Inputs
- Outputs
- Functional specification
- Timing specification


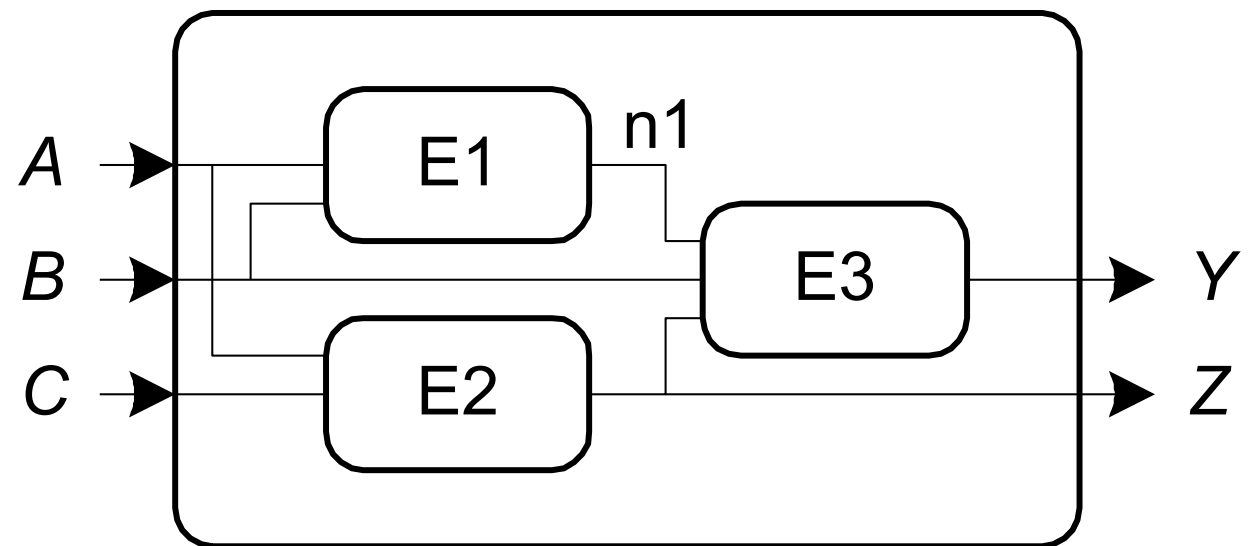
# Circuits

- Nodes
  - Inputs:  $A, B, C$
  - Outputs:  $Y, Z$
  - Internal:  $n1$
- Circuit elements
  - $E1, E2, E3$
  - Each a circuit



# Types of Logic Circuits

- **Combinational Logic**


- Memoryless
- Outputs determined by current values of inputs

- **Sequential Logic**

- Has memory
- Outputs determined by previous and current values of inputs
 
# Combinational Composition


- Every element is combinational
- Every node is either an input or connects to *exactly one* output
- The circuit contains no **cyclic paths**
- **Example:**


 
# Example

$$S = F(A, B, C_{\text{in}})$$

$$C_{\text{out}} = F(A, B, C_{\text{in}})$$



$$S = A \oplus B \oplus C_{\text{in}}$$

$$C_{\text{out}} = AB + AC_{\text{in}} + BC_{\text{in}}$$

# Design Procedure

- Specification
  - Write a specification for the circuit if one is not already available
- Formulation
  - Derive a truth table
- Optimization
  - Apply 2-level and multiple-level optimization
- Technology Mapping
  - Map the logic diagram to the implementation technology selected
- Verification
  - Verify the correctness of the final design manually or using simulation

# Example: BCD to Excess-3 Code Converter

- Specification
  - BCD code words for digits 0 through 9
    - 4-bit patterns 0000 to 1001, respectively
  - Excess-3 code words for digits 0 through 9
    - 4-bit patterns consisting of 3 (binary 0011) added to each BCD code word



# Example: BCD to Excess-3 Code Converter


- Formulation
  - Variables
    - BCD: A,B,C,D
  - Variables
    - Excess-3: W,X,Y,Z
  - Don't Cares
    - BCD 1010 to 1111

Input BCD A B C D	Output Excess-3 W X Y Z
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0

# Example: BCD to Excess-3 Code Converter


- Optimization

**z**

 


$$Z = D'$$

**y**

 


$$Y = CD + C'D'$$

**x**

 

$$W = B'C + B'D + BC'D'$$


**w**

 


$$W = A + BC + BD$$

# Example: BCD to Excess-3 Code Converter


- Technology Mapping

 


# Example: BCD-to-7-Segment Decoder

 

# Example: BCD-to-7-Segment Decoder

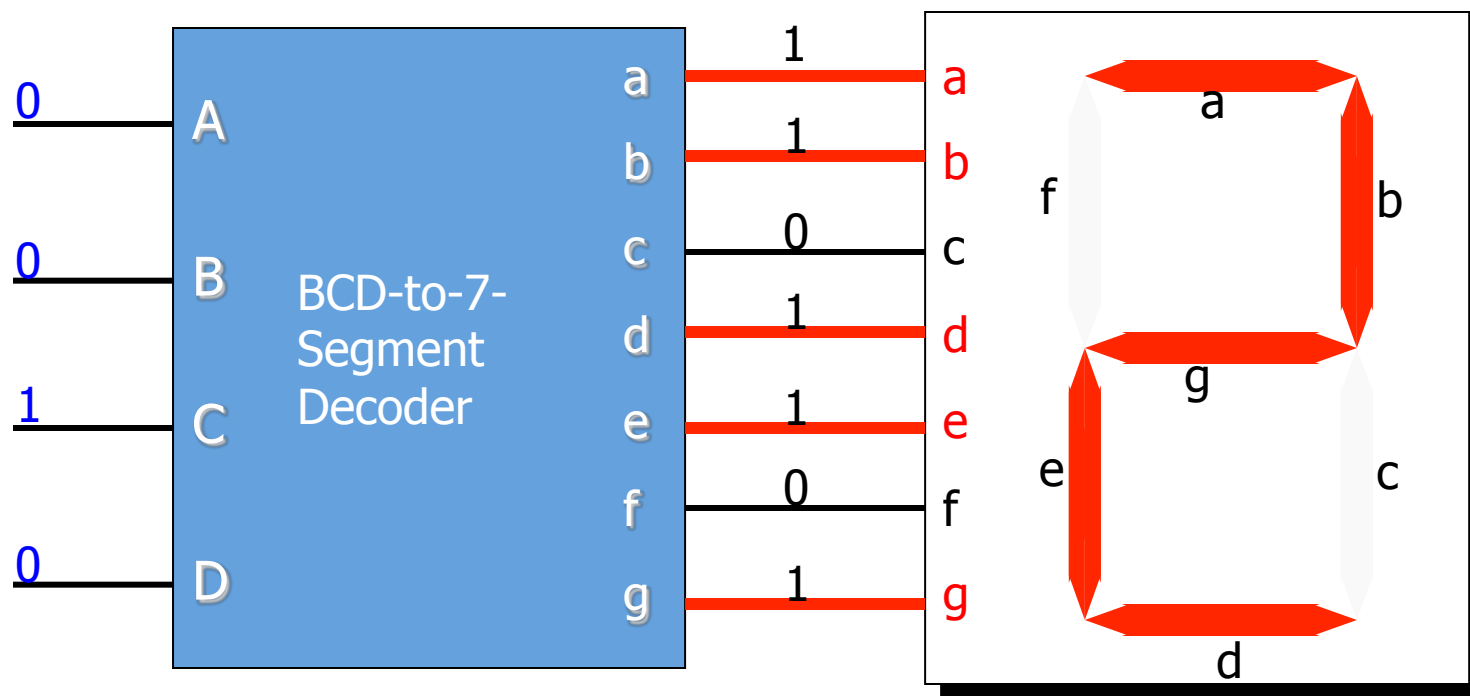

# Example: BCD-to-7-Segment Decoder

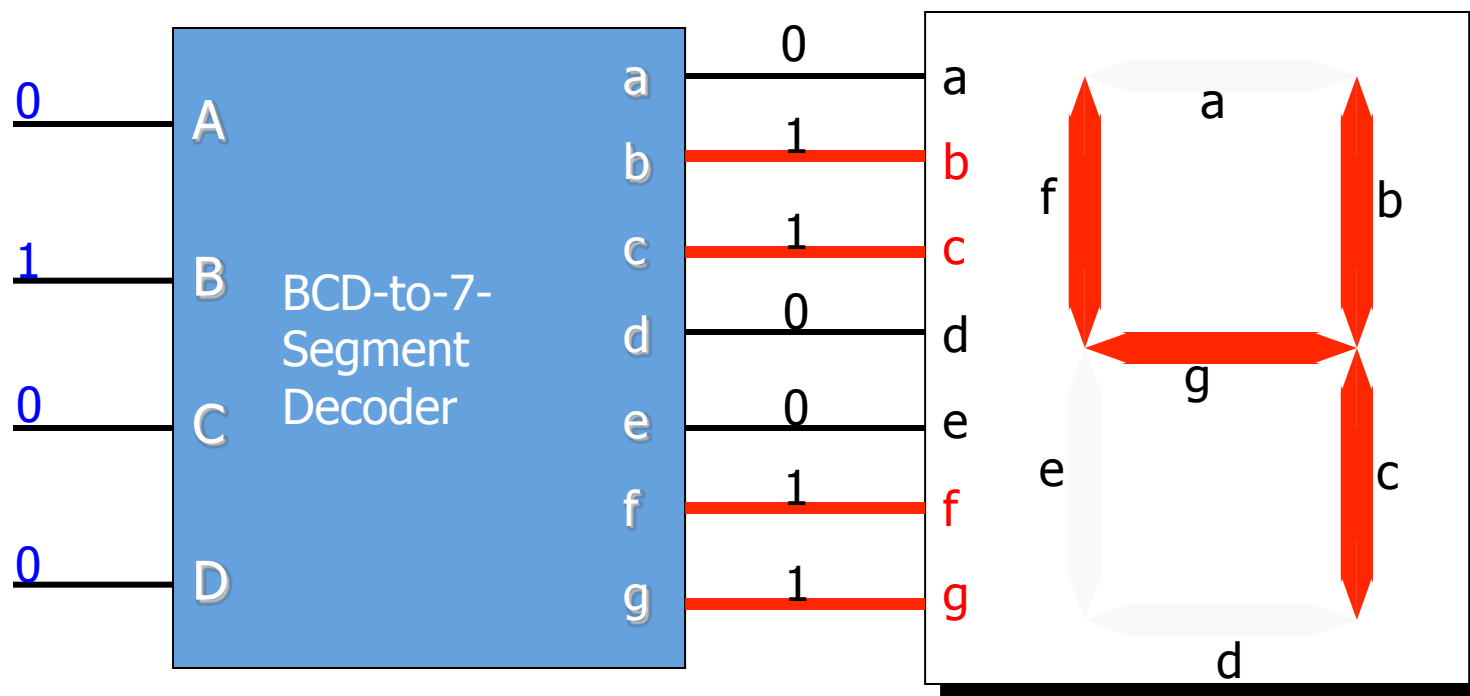

# Example: BCD-to-7-Segment Decoder

	A	B	C	D	a	b	c	d	e	f	g	
0	0	0	0	0	1	1	1	1	1	1	0	0
1	0	0	0	1	0	1	1	0	0	0	0	1
2	0	0	1	0	1	1	0	1	1	0	1	2
3	0	0	1	1	1	1	1	1	0	0	1	3
4	0	1	0	0	0	1	1	0	0	1	1	4
5	0	1	0	1	1	0	1	1	0	1	1	5
6	0	1	1	0	0	0	1	1	1	1	1	6
7	0	1	1	1	1	1	1	0	0	0	0	7
8	1	0	0	0	1	1	1	1	1	1	1	8
9	1	0	0	1	1	1	1	0	0	1	1	9
>10	All other inputs				0	0	0	0	0	0	0	

# Example: BCD-to-7-Segment Decoder

	A	B	C	D	a
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
>10	All other inputs				0

		CD			
AB		00	01	11	10
		00	01	11	10
	00	1	0	1	1
	01	0	1	1	0
	11	0	0	0	0
	10	1	1	0	0

$$a = \overline{A}\overline{B}\overline{D} + \overline{A}CD + \overline{A}BD + A\overline{B}\overline{C}$$



# Example: BCD-to-7-Segment Decoder



	A	B	C	D	b
0	0	0	0	0	1
1	0	0	0	1	1
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
>10	All other inputs				0

	CD	00	01	11	10
AB	00	1	1	1	1
	01	1	0	1	0
	11	0	0	0	0
	10	1	1	0	0


$$b = \overline{B}\overline{C} + \overline{A}\overline{B} + \overline{A}\overline{C}\overline{D} + \overline{A}\overline{C}D$$

# NAND Mapping Algorithm



- Replace ANDs and ORs:

  

# NAND Mapping Example

 


# NAND Mapping Example

  


# NOR Mapping Example

- Replace ANDs and ORs:

 

# NOR Mapping Example

 

# NOR Mapping Example

