


Counters, Shift Registers, Memory Arrays

Digital Computer Design


Counters

- Increments on each clock edge
- Used to cycle through numbers. For example,
 - 000, 001, 010, 011, 100, 101, 110, 111, 000, 001...
- Example uses:
 - Digital clock displays

Symbol

 


Implementation

 


Shift Registers

- Shift a new bit in on each clock edge
- Shift a bit out on each clock edge
- *Serial-to-parallel converter*: converts serial input (S_{in}) to parallel output ($Q_{0:N-1}$)

Symbol:

 


Implementation:

 


Shift Register with Parallel Load

 - When $Load = 1$, acts as a normal N -bit register
- When $Load = 0$, acts as a shift register
- Now can act as a *serial-to-parallel converter* (S_{in} to $Q_{0:N-1}$) or a *parallel-to-serial converter* ($D_{0:N-1}$ to S_{out})





Memory Arrays

 - Efficiently store large amounts of data
- 3 common types:
 - Dynamic random access memory (DRAM)
 - Static random access memory (SRAM)
 - Read only memory (ROM)
- M -bit data value **read/written** at each unique N -bit address



Memory Arrays

  
- 2-dimensional array of bit cells
- Each bit cell stores one bit
- N address bits and M data bits:
 - 2^N rows and M columns
 - **Depth:** number of rows (number of words)
 - **Width:** number of columns (size of word)
 - **Array size:** depth \times width = $2^N \times M$




Address	Data			
11	0	1	0	depth ↑ ↓
10	1	0	0	
01	1	1	0	
00	0	1	1	
	width ←→			

Memory Array Example

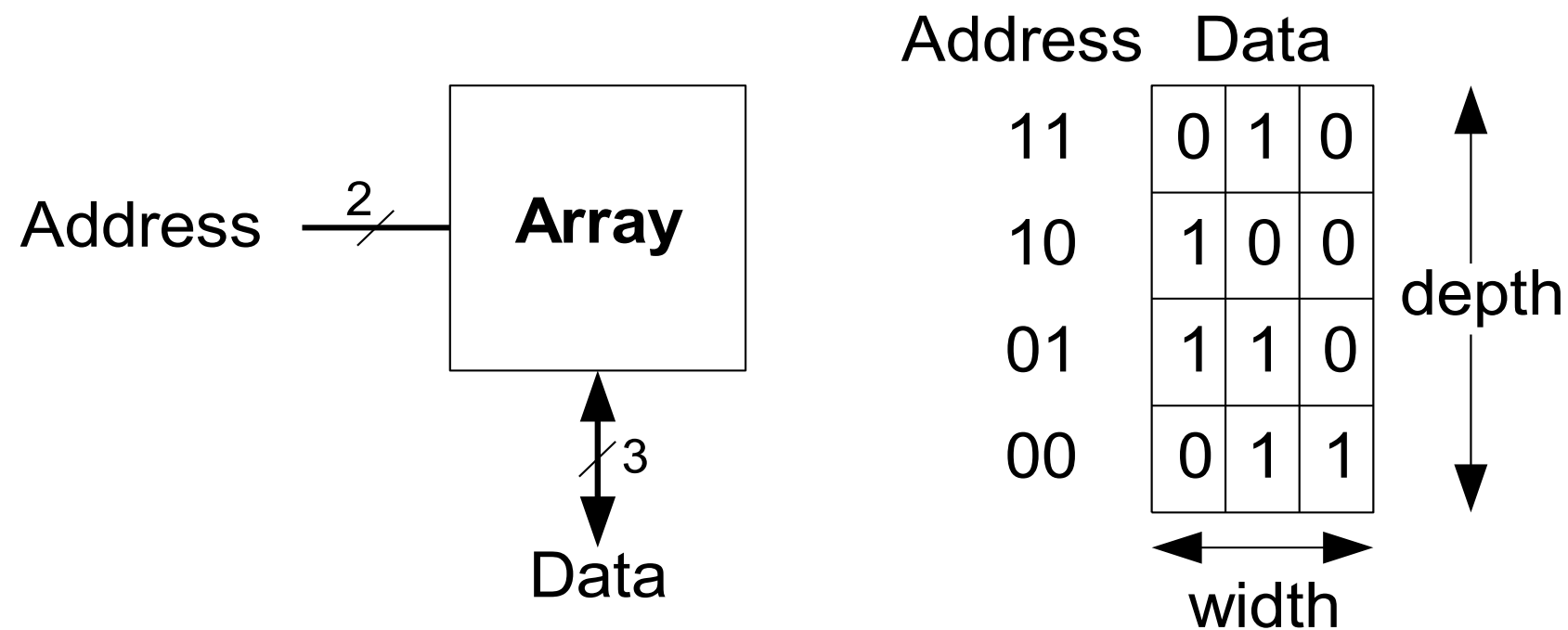- $2^2 \times 3$ -bit array
- Number of words: 4
- Word size: 3-bits
- For example, the 3-bit word stored at address 10 is 100



Memory Arrays

 


How many words? Word size?

Addressing Memory

Let's implement a simple memory array with:

- 3-bit addressability & address space size of 2 (total of 6 bits)

1 Bit

 


6-Bit Memory Array

	Bit ₂	Bit ₁	Bit ₀
Addr(0)			
Addr(1)			

Reading from Memory

How can we select the address to read?

 - Because there are 2 addresses, address size is $\log(2)=1$ bit




Reading from Memory

How can we select the address to read?

- Because there are 2 addresses, address size is $\log(2)=1$ bit


Addr[0]

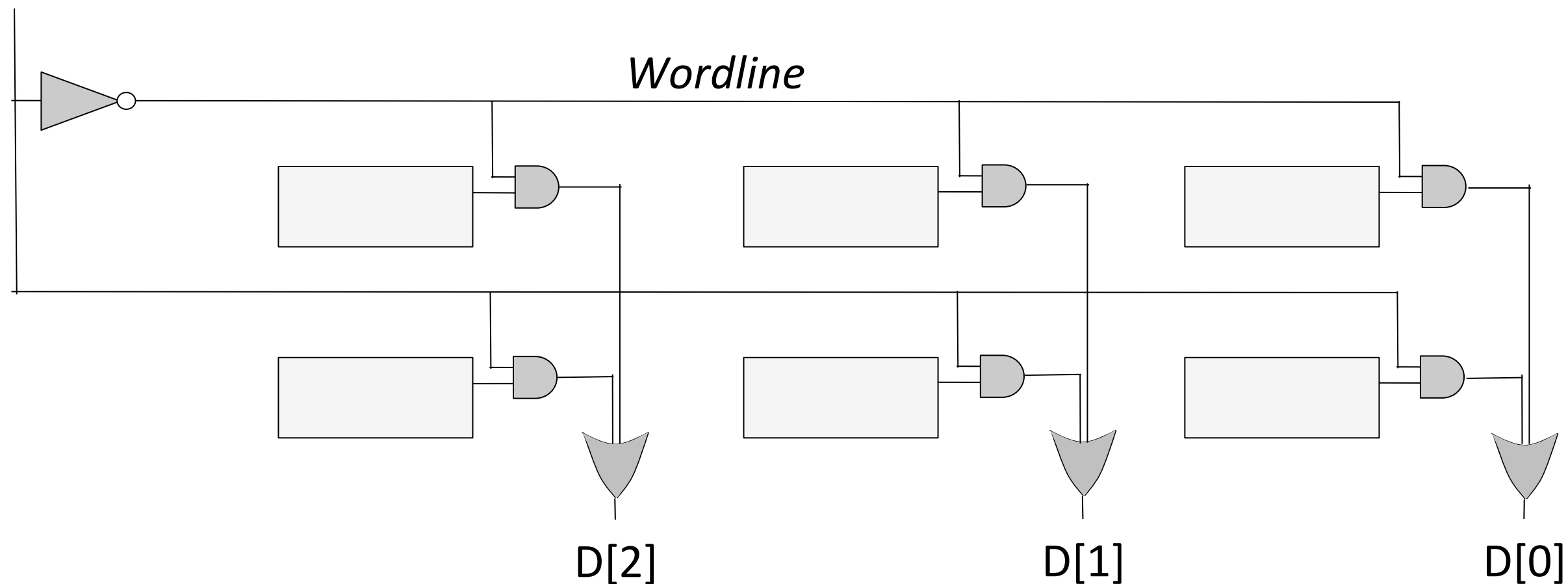

Reading from Memory

How can we select the address to read?

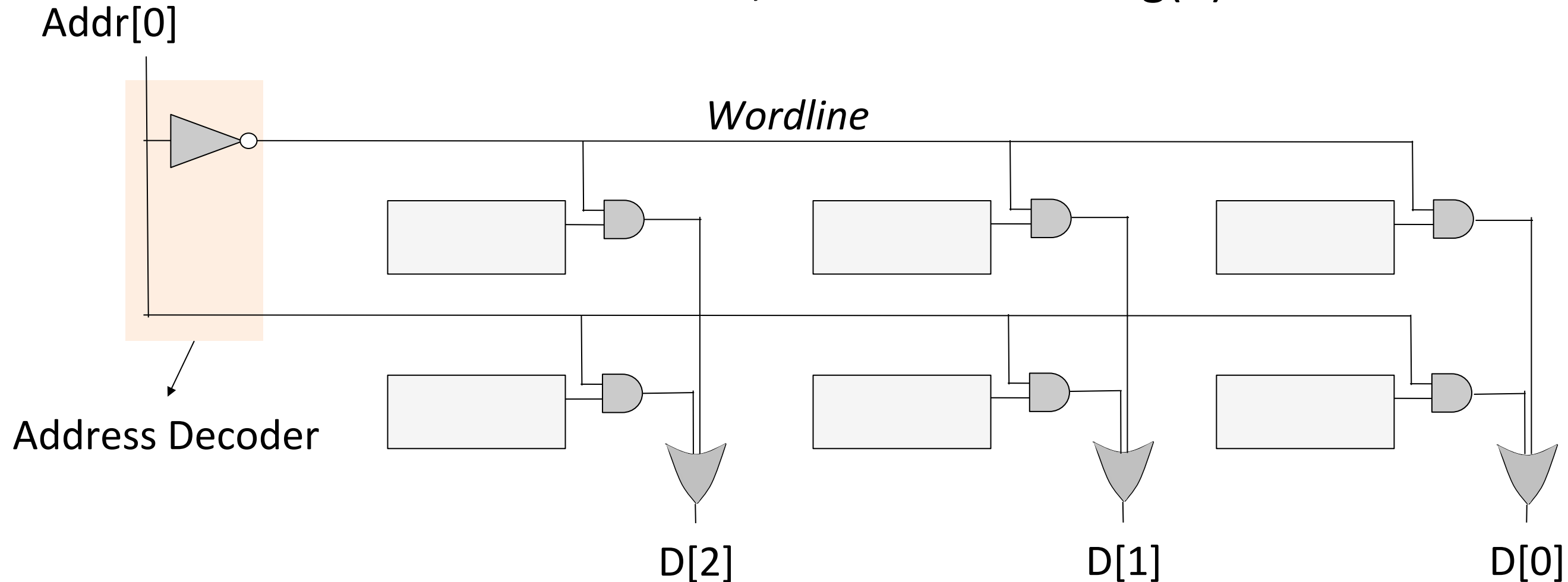
- Because there are 2 addresses, address size is $\log(2)=1$ bit



Reading from Memory


How can we select the address to read?

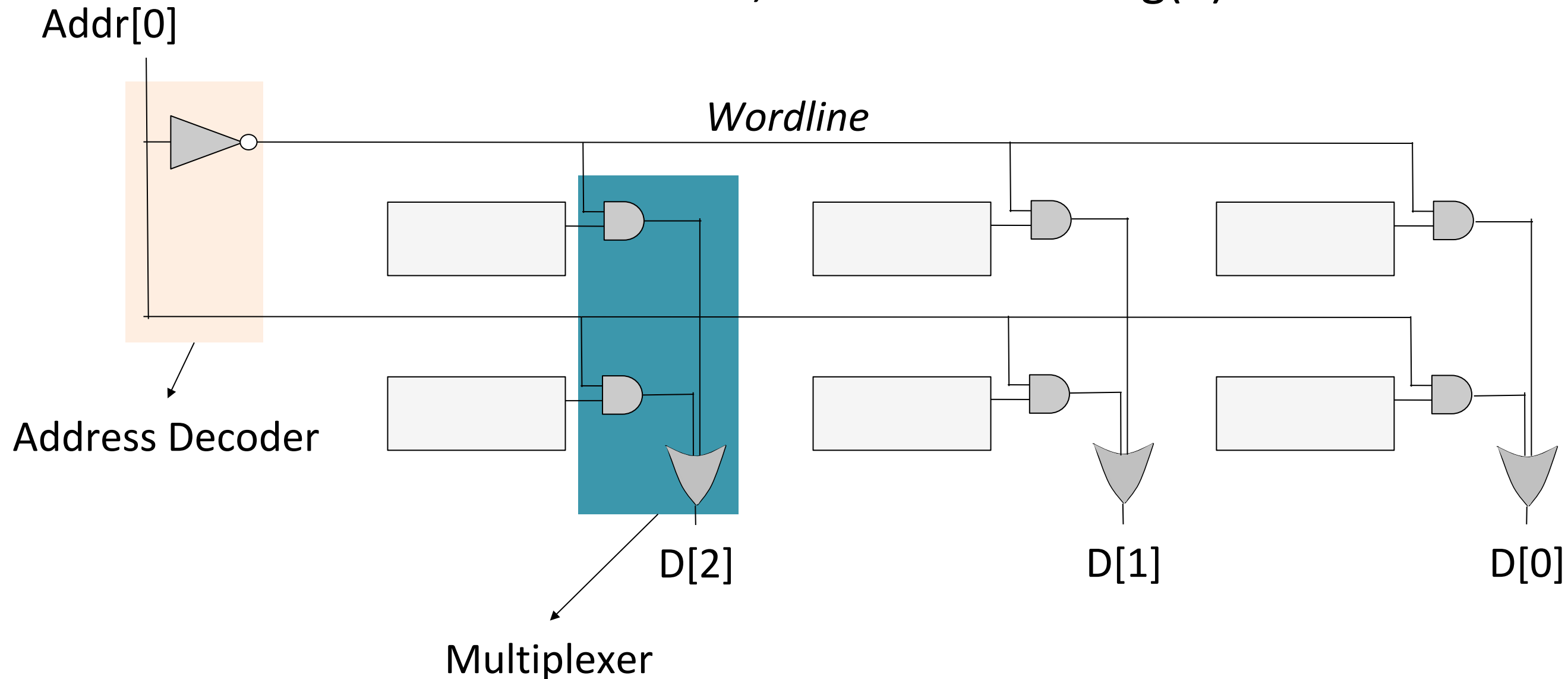- Because there are 2 addresses, address size is $\log(2)=1$ bit



Writing to Memory

 
How can we select the address and write to it?



Writing to Memory


How can we select the address and write to it?

- Input is indicated with D_i

 


Putting it all Together

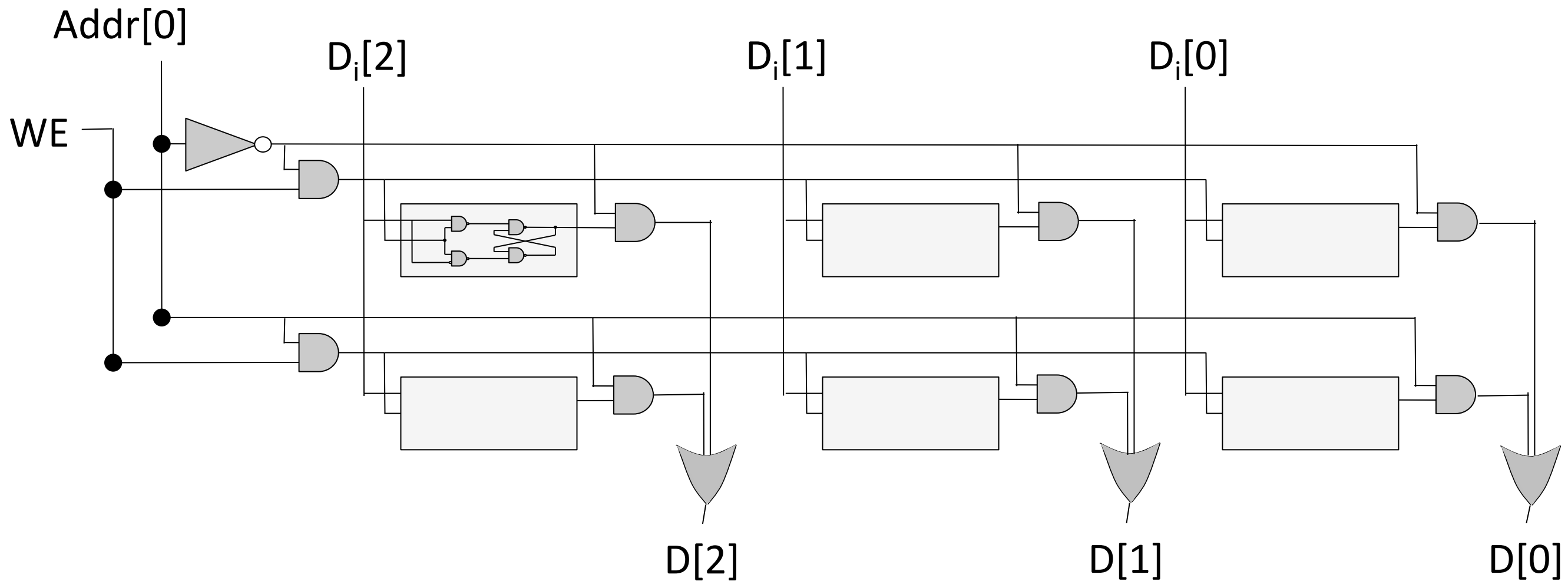
Enable reading and writing to a memory array



A Bigger Memory Array

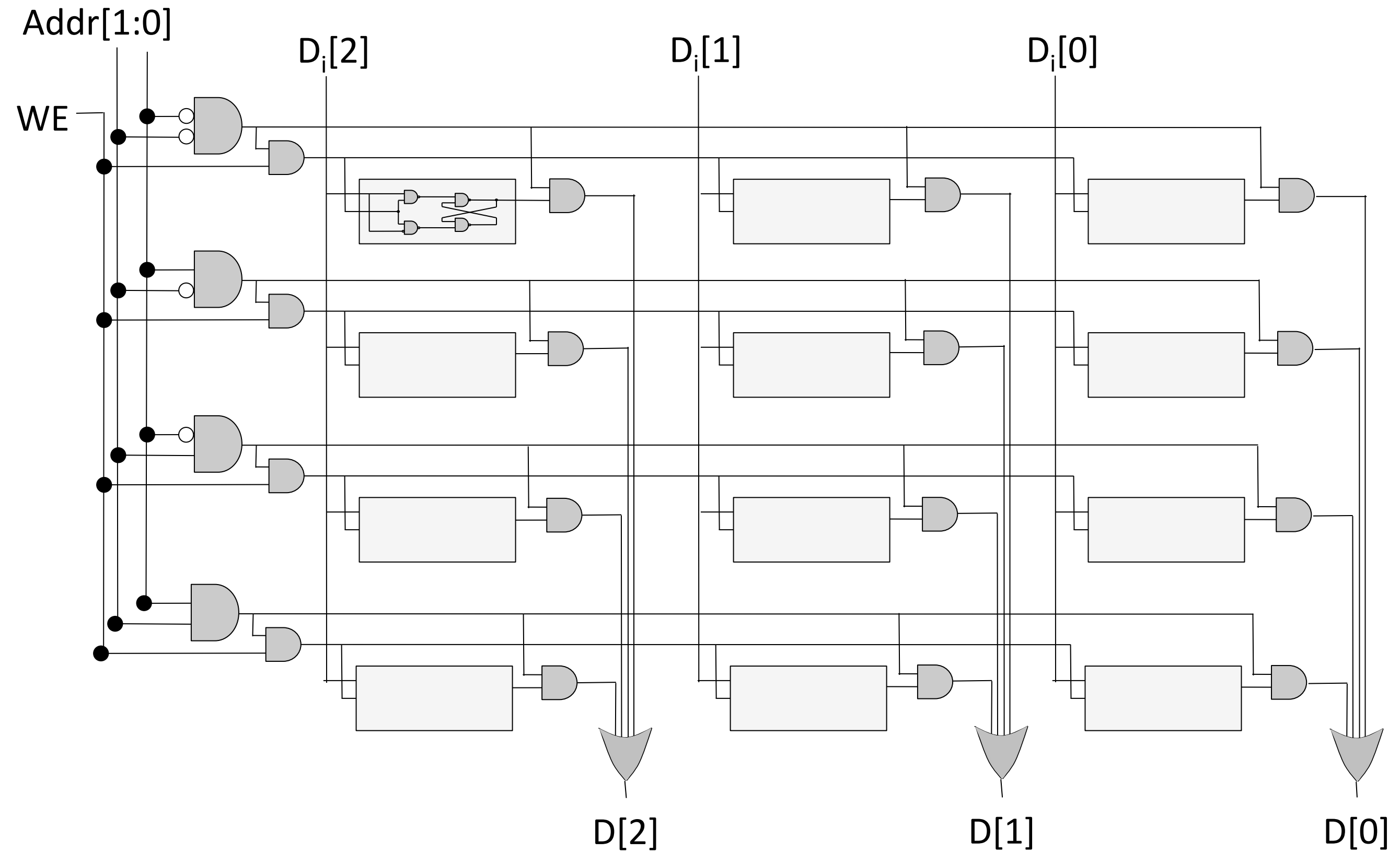


A Bigger Memory Array

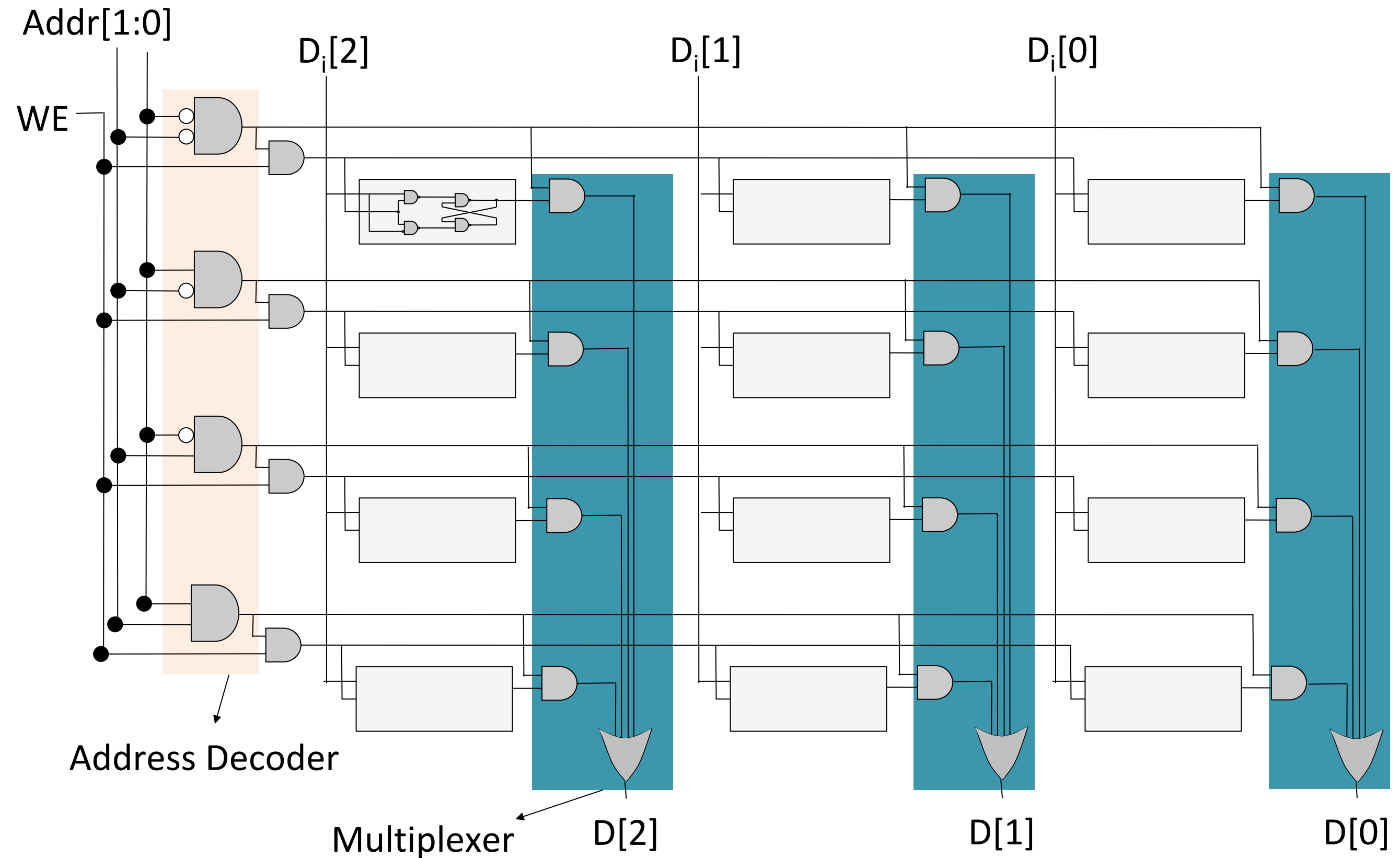

Multi-ported Memories

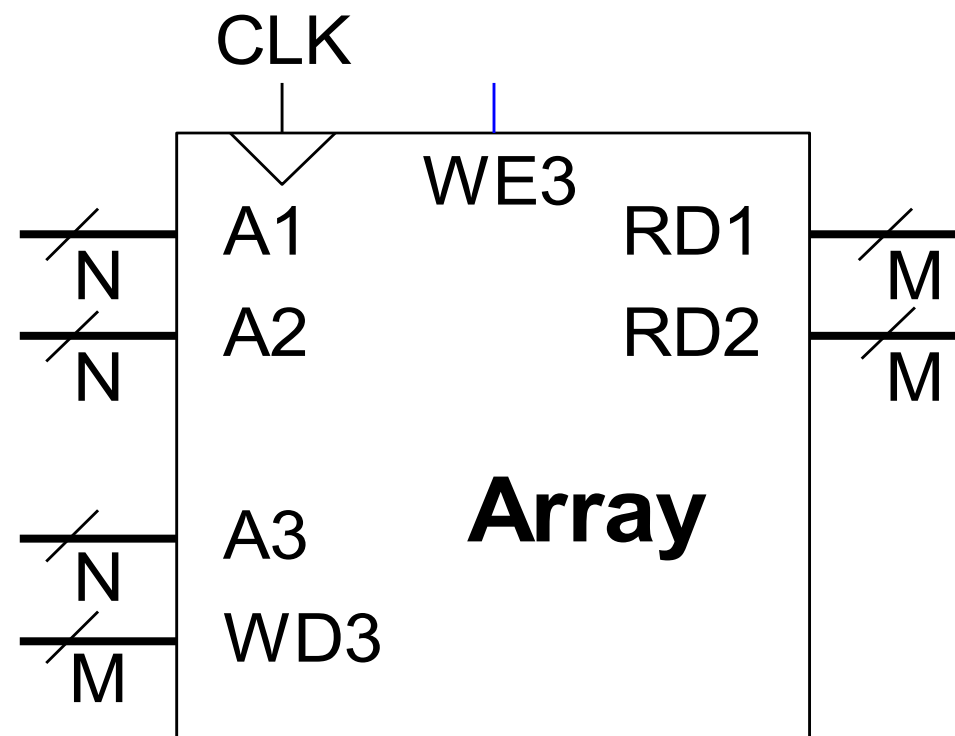- Multiported memories can access several addresses **simultaneously**
- Example: 3-ported memory
 - 2 read ports (A1/RD1, A2/RD2)
 - 1 write port (A3/WD3, WE3 enables writing)
- **Register file:** small multi-ported memory



Types of Memory


- Memories are classified based on how they store bits in the bit cell.
 - Random access memory (RAM):
 - **volatile:** loses its data when power off
 - called random access memory because any data word is accessed with the same delay as any other.
 - e.g. main memory in computers
 - Read only memory (ROM):
 - **nonvolatile:** retains data when power off
 - e.g. flash memory in cameras

Types of RAM

- **DRAM** (Dynamic random access memory)
- **SRAM** (Static random access memory)
- Differ in how they store data:
 - DRAM uses a **capacitor**
 - SRAM uses **cross-coupled inverters**



Dynamic Random Access Memory (DRAM)

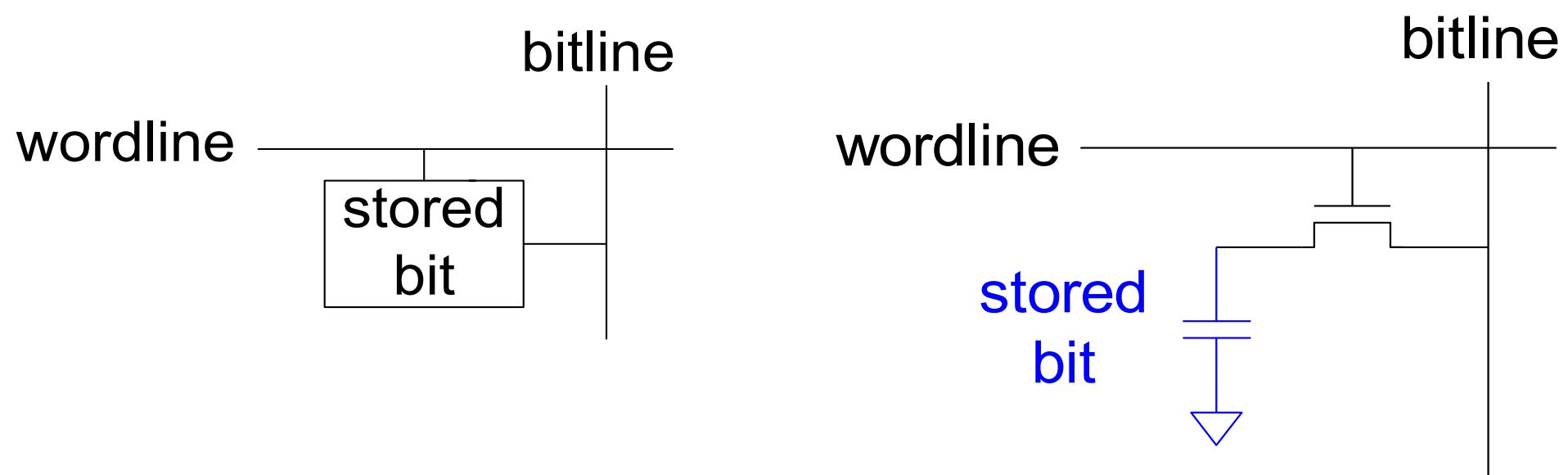- Data bits stored on **capacitor**
 - When the capacitor is charged to V_{DD} the stored bit is 1
 - When it is discharged to GND the stored bit is 0
- The transistor behaves as a **switch**
 - either connects or disconnects the capacitor from the bitline.



Dynamic Random Access Memory (DRAM)

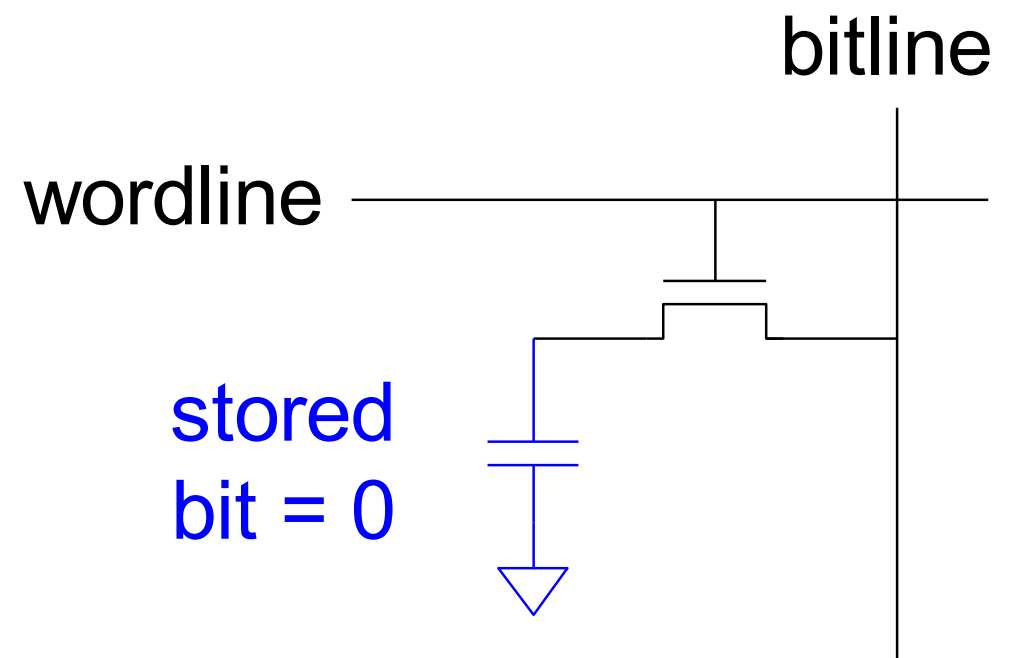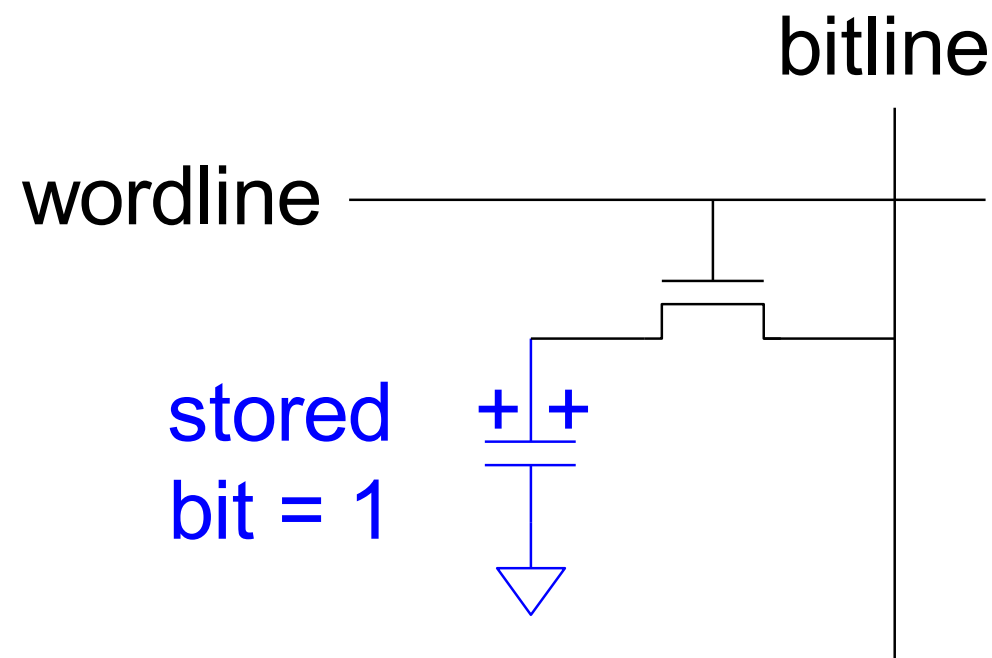
- **Dynamic** because the value needs to be **refreshed** (rewritten) periodically and after read:
 - Charge leakage from the capacitor degrades the value
 - Reading destroys the stored value
 - Data word must be restored (rewritten) after each read.




Static Random Access Memory (SRAM)

- Static because stored bits do not need to be refreshed.
 - Unlike DRAM, if noise degrades the value of the stored bit, the cross-coupled inverters restore the value.

DRAM bit cell:

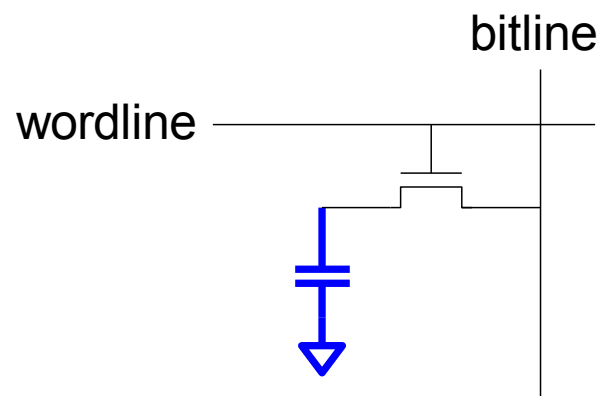

SRAM bit cell:

 

Area and Delay



- The data bit stored in a flip-flop is available immediately at its output.
 - But flip-flops take at least 20 transistors to build.
- DRAM latency is longer than that of SRAM
 - Because its bitline is not actively driven by a transistor.
 - DRAM must wait for charge to move (relatively) slowly from the capacitor to the bitline.

Memory Type	Transistors per Bit Cell	Latency
flip-flop	~20	fast
SRAM	6	medium
DRAM	1	slow

Read Only Memory ROM



- Read only memory (ROM) stores a bit as the presence or absence of a transistor.
 - If the transistor is present, it pulls the bitline LOW.
 - If it is absent, the bitline remains HIGH.

  The contents of the ROM bit are specified during **manufacturing** by the presence or absence of a transistor in each bit cell.



Read Only Memory ROM

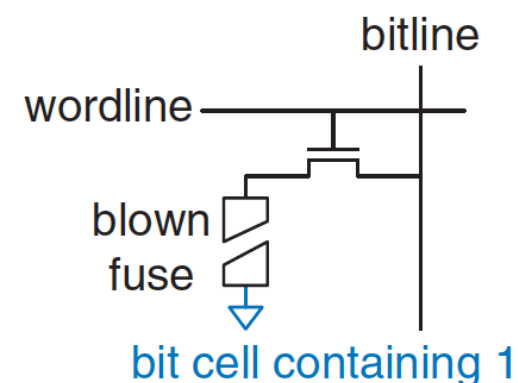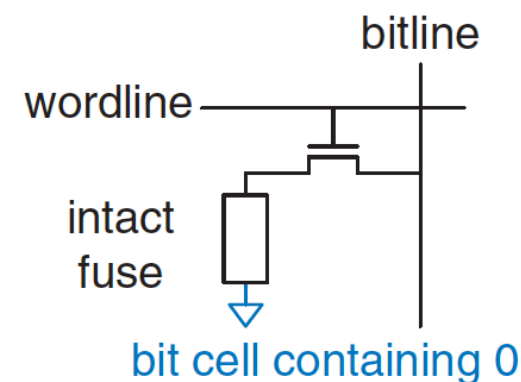
- A **programmable ROM (PROM)** places a transistor in every bit cell
 - but provides a way to connect or disconnect the transistor to ground.
- A **fuse-programmable ROM** allows user programs to selectively blow fuses by applying a high voltage.



Read Only Memory ROM

- Erasable PROMs (EPROMs) replace the transistor and fuse with a *floating-gate transistor*.
 - The floating gate is not physically attached to any other wires.
 - When suitable high voltages are applied, transistor is connects to the bitline to the wordline.
 - When the EPROM is exposed to intense ultraviolet (UV) light for about half an hour, the transistor is disconnected.
 - These actions are called **programming** and **erasing**, respectively.


Read Only Memory ROM: Dot Notation

 

Address	Data			depth ↑ ↓
11	0	1	0	
10	1	0	0	
01	1	1	0	
00	0	1	1	
width ←→				

Logic with Memory Arrays

 - Although they are used primarily for data storage, memory arrays can also perform **combinational logic functions**.
- A 2^N -word x M-bit memory can perform any combinational function of **N inputs** and **M outputs**.



$$X = AB$$


$$Y = A + B$$

$$Z = A \bar{B}$$


Logic with Memory Arrays

- Called *lookup tables (LUTs)*: look up output at each input combination (address)

Truth Table		
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

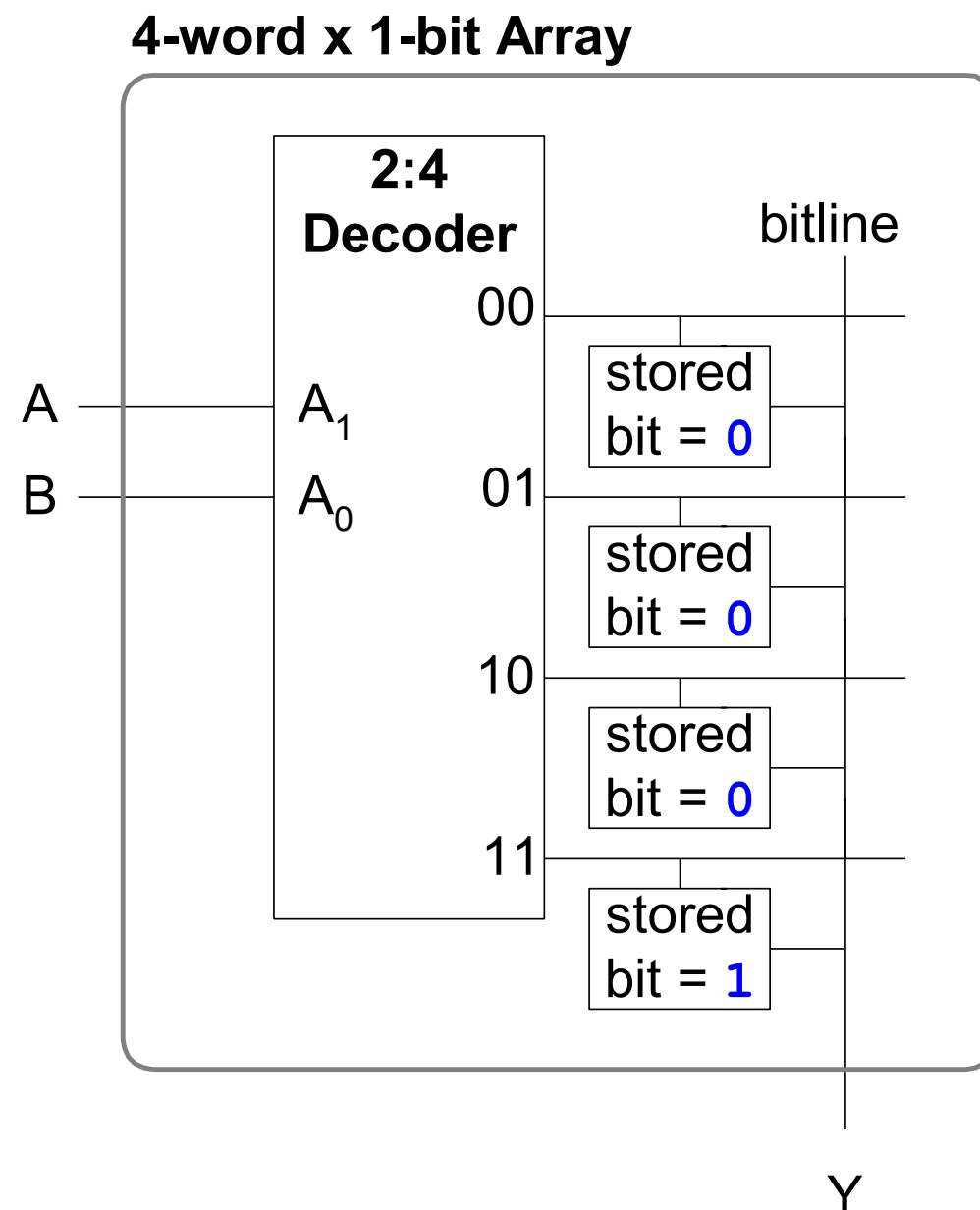

Logic with Memory Arrays

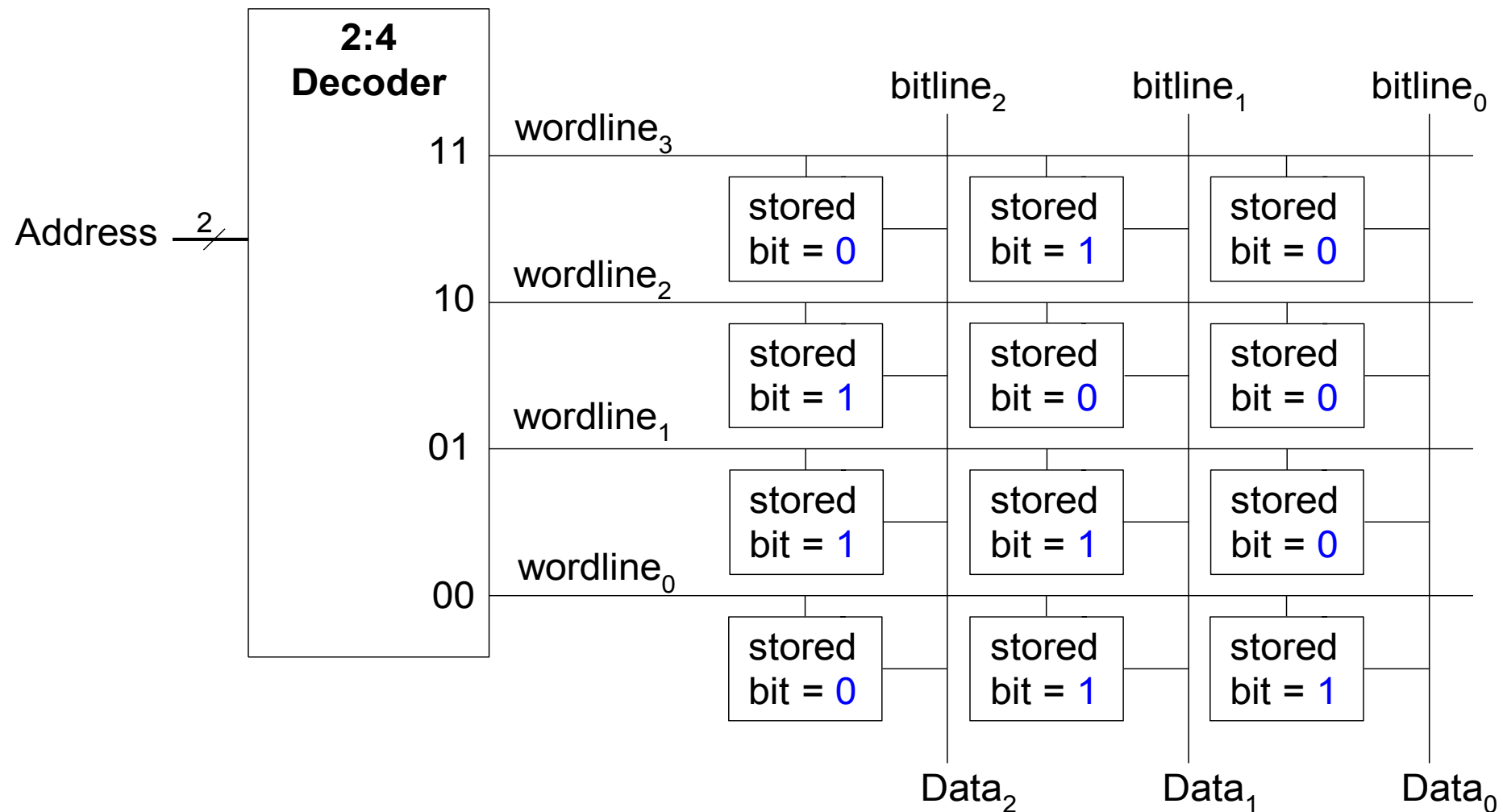

$$\text{Data}_2 = A_1 \text{ xor } A_0$$

$$\text{Data}_1 = \bar{A}_1 + A_0$$

$$\text{Data}_0 = \bar{A}_1 \bar{A}_0$$

Further Reading

- You can read **Chapter 5** of your book
–**Sections 5.4 and 5.5**

