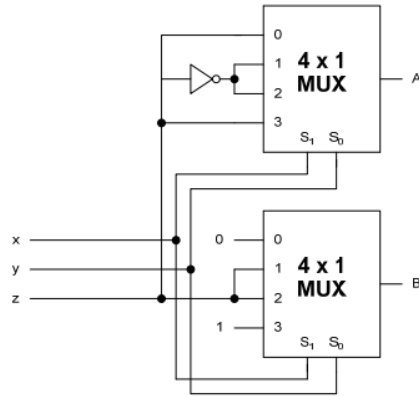


## Logic Design – Homework 7

**(1)** Express the A and B outputs of the following circuit as sum-of-minterms.



**(2)** Design the following functions with **(a)** a multiplexer and **(b)** a decoder.

**(I)**  $X(A,B,C) = \sum(0,1,2,6,7)$

**(II)**  $Y(A,B,C) = \sum(2,3,4,5,6)$

**(III)**  $F(A,B,C,D) = \sum(0,1,4,7,9,12)$

**(IV)**  $F(x,y,z) = \sum m(2,5,6,7)$

**(V)**  $F = \sum(2,4,6,9,10,15)$

**(VI)**  $F(W,X,Y,Z) = \sum m(2,3,6,7,9,11,13,15)$

**(VII)**  $F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 14)$

**(VIII)**  $F(X, Y, Z) = XY' + YZ$

**(IX)**  $F(X, Y, Z) = XY' + X'Y'Z$

**(X)**  $F(x,y,z) = y'z' + xy' + yz'$

**(3)** A combinational circuit is defined by the following Boolean functions. Design the circuit with a decoder and external gates.

$$F1 = x'y'z' + xz$$

$$F2 = xy'z' + x'y$$

**(4)** Using a multiplexer, design a combinatorial circuit that outputs 1 if the 4-bit input is a prime number.

**(5)** Using a decoder, design a combinatorial circuit that outputs the excess-3 code of the 3-bit input.

**(6)** Using a multiplexer, design a combinatorial circuit that calculates the even parity of a 4-bit number.

**(7)** Design a 16x1 multiplexer using two 8x1 multiplexer and one 2x1 multiplexer.