

Logic Gates


Logic Design

Logic Gates

- **Perform logic functions:**
 - inversion (NOT), AND, OR, NAND, NOR, etc.
- **Single-input:**
 - NOT gate, buffer
- **Two-input:**
 - AND, OR, XOR, NAND, NOR, XNOR
- **Multiple-input**

Single-Input Logic Gates


NOT

 

$$Y = \overline{A}$$

A	Y
0	1
1	0

BUF

 


$$Y = A$$

A	Y
0	0
1	1

Two-Input Logic Gates


AND

 

$$Y = AB$$

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	0
1	0	0
1	1	1

OR

 


$$Y = A + B$$

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	1
1	0	1
1	1	1

More Two-Input Logic Gates


XOR

 

$$Y = A \oplus B$$

A	B	Y
0	0	
0	1	
1	0	
1	1	


NAND

 

$$Y = \overline{AB}$$

A	B	Y
0	0	
0	1	
1	0	
1	1	


NOR

 

$$Y = \overline{A + B}$$

A	B	Y
0	0	
0	1	
1	0	
1	1	

XNOR

 


$$Y = \overline{A \oplus B}$$

A	B	Y
0	0	
0	1	
1	0	
1	1	

Multiple-Input Logic Gates


NOR3

 

$$Y = \overline{A+B+C}$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

AND3

 

$$Y = ABC$$


A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Logic Levels

- Discrete voltages represent 1 and 0
- For example:
 - 0 = *ground* (GND) or 0 volts
 - 1 = V_{DD} or 5 volts
- What about 4.99 volts? Is that a 0 or a 1?
- What about 3.2 volts?

What is Noise?

 - **Anything that degrades the signal**
 - E.g., resistance, power supply noise, coupling to neighboring wires, etc.
- **Example:** a gate (driver) outputs 5 V but, because of resistance in a long wire, receiver gets 4.5 V




The Static Discipline

- With logically valid inputs, every circuit element must produce logically valid outputs
- Use limited ranges of voltages to represent discrete values
 - The driver produces a **LOW** (0) output in the range of 0 to V_{OL}
 - The driver produces a **HIGH** (1) output in the range of V_{OH} to V_{DD} .
 - If the receiver gets an input in the range of 0 to V_{IL} , it will consider the input to be **LOW** (0) .
 - If the receiver gets an input in the range of V_{IH} to V_{DD} , it will consider the input to be **HIGH** (1) .

The Static Discipline



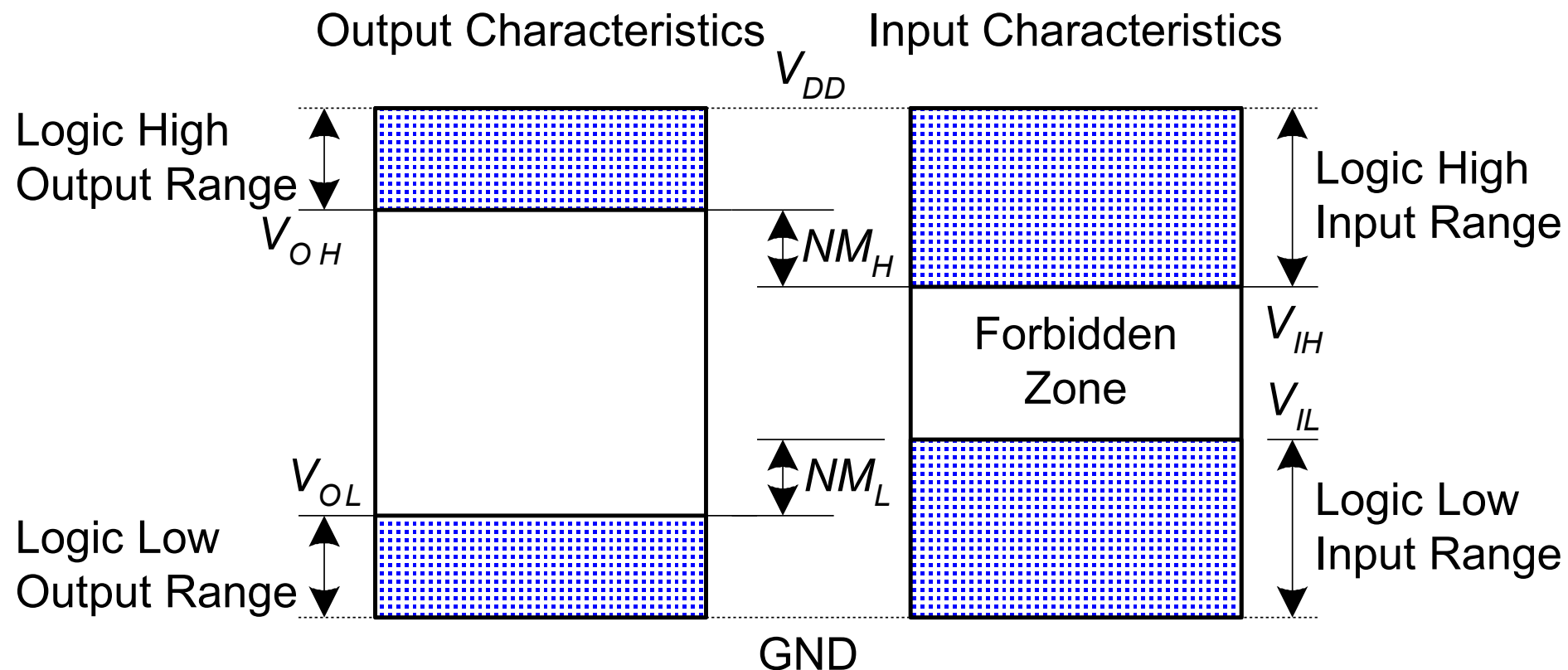
The **noise margin** is the amount of noise that could be added to a worst-case output such that the signal can still be interpreted as a valid input.



High Noise Margin: $NM_H = V_{OH} - V_{IH}$


Low Noise Margin: $NM_L = V_{IL} - V_{OL}$

DC Transfer Characteristics

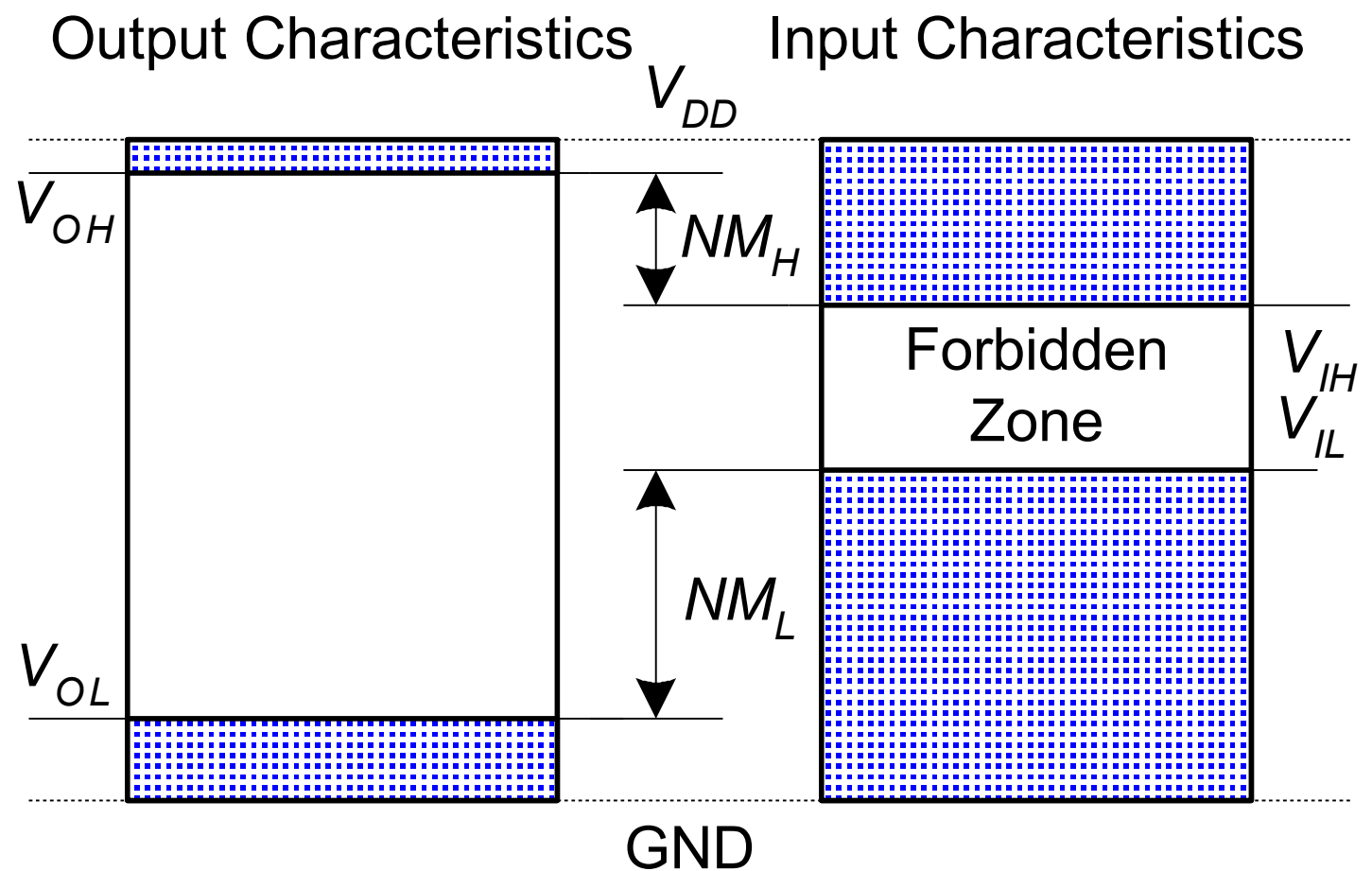  


V_{DD} Scaling

 - In 1970's and 1980's, $V_{DD} = 5\text{ V}$
- V_{DD} has dropped
 - Avoid frying tiny transistors
 - Save power
- 3.3 V, 2.5 V, 1.8 V, 1.5 V, 1.2 V, 1.0 V...
 - Be careful connecting chips with different supply voltages



7408 Quad 2 Input AND

 


Logic Family Examples


Logic Family	V_{DD}	V_{IL}	V_{IH}	V_{OL}	V_{OH}
TTL	5 (4.75 - 5.25)	0.8	2.0	0.4	2.4
CMOS	5 (4.5 - 6)	1.35	3.15	0.33	3.84
LVTTL	3.3 (3 - 3.6)	0.8	2.0	0.4	2.4
LVC MOS	3.3 (3 - 3.6)	0.9	1.8	0.36	2.7

Transistors

 
- Logic gates built from transistors
- 3-ported voltage-controlled switch
 - 2 ports connected depending on voltage of 3rd
 - d and s are connected (ON) when g is 1



$g = 0$

 

$g = 1$

 


Robert Noyce, 1927-1990

- Nicknamed “Mayor of Silicon Valley”
- Cofounded Fairchild Semiconductor in 1957
- Cofounded Intel in 1968
- Co-invented the integrated circuit





Silicon

 - Transistors built from silicon, a semiconductor
- Pure silicon is a poor conductor (no free charges)
- Doped silicon is a good conductor (free charges)
 - If arsenic (As) is added - an extra electron
 - If boron (B) is added - missing an electron (a hole)
 - n-type (free **n**egative charges, electrons)
 - p-type (free **p**ositive charges, holes)



MOS Transistors

  - **Metal oxide silicon (MOS) transistors:**
 - Polysilicon (used to be **metal**) gate
 - **Oxide** (silicon dioxide) insulator
 - Doped **silicon**




nMOS

Transistors: nMOS


Gate = 0

 OFF (no connection between source and drain)



Gate = 1


ON (channel between source and drain)

 

Transistors: pMOS


pMOS transistor is opposite

 - ON when **Gate = 0**
- OFF when **Gate = 1**




Transistor Function



nMOS

 



pMOS

 

$g = 0$

  


$g = 1$

  


Transistor Function

 - **nMOS**: pass good **0**'s, so connect source to GND
- **pMOS**: pass good **1**'s, so connect source to V_{DD}




CMOS Gates: NOT Gate

NOT

 

$$Y = \overline{A}$$


<i>A</i>	<i>Y</i>
0	1
1	0

 

<i>A</i>	P1	N1	<i>Y</i>
0	ON	OFF	1
1	OFF	ON	0


CMOS Gates: NAND Gate

NAND

 

$$Y = \overline{AB}$$


<i>A</i>	<i>B</i>	<i>Y</i>
0	0	1
0	1	1
1	0	1
1	1	0

 

<i>A</i>	<i>B</i>	<i>P1</i>	<i>P2</i>	<i>N1</i>	<i>N2</i>	<i>Y</i>
0	0	ON	ON	OFF	OFF	1
0	1	ON	OFF	OFF	ON	1
1	0	OFF	ON	ON	OFF	1
1	1	OFF	OFF	ON	ON	0


NOR3 Gate

 How do you build a three-input NOR gate? (NOR3)




AND2 Gate

How do you build a two-input AND gate?

 


Gordon Moore, 1929-

 - Cofounded Intel in 1968 with Robert Noyce.
- **Moore's Law:** number of transistors on a computer chip doubles every year (observed in 1965)
- Since 1975, transistor counts have doubled every two years.



Moore's Law

 

“If the automobile had followed the same development cycle as the computer, a Rolls-Royce would today cost \$100, get one million miles to the gallon, and explode once a year . . .” (Robert Cringely, Infoworld)

– Robert Cringley

Power Consumption

Power = Energy consumed per unit time

- Dynamic power consumption
- Static power consumption

Dynamic Power Consumption

- **Power to charge transistor gate capacitances**
 - Energy required to charge a capacitance, C , to V_{DD} is CV_{DD}^2
 - Circuit running at frequency f : transistors switch (from 1 to 0 or vice versa) at that frequency
 - Capacitor is charged $f/2$ times per second (discharging from 1 to 0 is free)
- **Dynamic power consumption:** $P_{dynamic} = \frac{1}{2}CV_{DD}^2f$

Static Power Consumption

- Power consumed when no gates are switching
- Caused by the *quiescent supply current*, I_{DD} (also called the *leakage current*)
- Static power consumption: $P_{static} = I_{DD}V_{DD}$

Power Consumption Example

- Estimate the power consumption of a wireless handheld computer

$$-V_{DD} = 1.2 \text{ V}$$

$$-C = 20 \text{ nF}$$

$$-f = 1 \text{ GHz}$$

$$-I_{DD} = 20 \text{ mA}$$

$$P = \frac{1}{2}CV_{DD}^2f + I_{DD}V_{DD}$$

$$= \frac{1}{2}(20 \text{ nF})(1.2 \text{ V})^2(1 \text{ GHz}) + (20 \text{ mA})(1.2 \text{ V})$$

$$= (14.4 + 0.024) \text{ W} \approx 14.4 \text{ W}$$