

# **Arithmetic/Logical Unit (ALU)**


Digital Computer Design

# Arithmetic Circuits

- Arithmetic circuits are the **central building blocks** of computers.
- Computers and digital logic perform many arithmetic functions:
  - addition, subtraction, comparisons, shifts, multiplication and division

# 1-Bit Adders


## Half Adder

 

A	B	C <sub>out</sub>	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$
$$C_{\text{out}} = AB$$

## Full Adder

 


C <sub>in</sub>	A	B	C <sub>out</sub>	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{\text{in}}$$
$$C_{\text{out}} = AB + AC_{\text{in}} + BC_{\text{in}}$$
 
# Multibit Adders - Carry Propagate Adders (CPAs)


- An **N-bit adder** sums two *N-bit* inputs A and B, and a carry in  $C_{in}$  to produce an *N-bit* result S and a carry out  $C_{out}$ .



- Multibit adder is commonly called a **carry propagate adder (CPA)**
  - because the carry out of one bit propagates into the next bit.
 
# CPAs: Ripple-Carry Adder


- Chain together N full adders.
  - The  $C_{out}$  of one stage acts as the  $C_{in}$  of the next stage



- The ripple-carry adder is **slow** when N is large.
  - For an 32-bit adder,  $S_{31}$  depends on  $C_{30}$ , which depends on  $C_{29}$ , which depends on  $C_{28}$ , and so forth all the way back to  $C_{in}$ .
 
# CPAs: Ripple-Carry Adder

- The fundamental reason that large ripple-carry adders are **slow** is that *the carry signals must propagate through every bit in the adder.*




$$\text{tripple} = Nt_{FA}$$

where  $t_{FA}$  is the delay of a 1-bit full adder


# Subtractor

- Subtraction is almost as easy:
  - flip the sign of the second number, then add.

## Symbol

 

## Implementation

 


- Flipping the sign of **a two's complement** number is done by inverting the bits and adding 1.


# Comparator: Equality

- A comparator determines whether two binary numbers are **equal** or if one is **greater** or **less than** the other.

## Symbol

 


## Implementation

 


 
# Comparator: Less Than


- Compute  $A - B$  and looking at **the sign** (most significant bit) of the result.
  - If the result is negative (i.e., the sign bit is 1), then  $A$  is less than  $B$ . Otherwise  $A$  is greater than or equal to  $B$ .



- This comparator, however, functions **incorrectly** upon **overflow**.
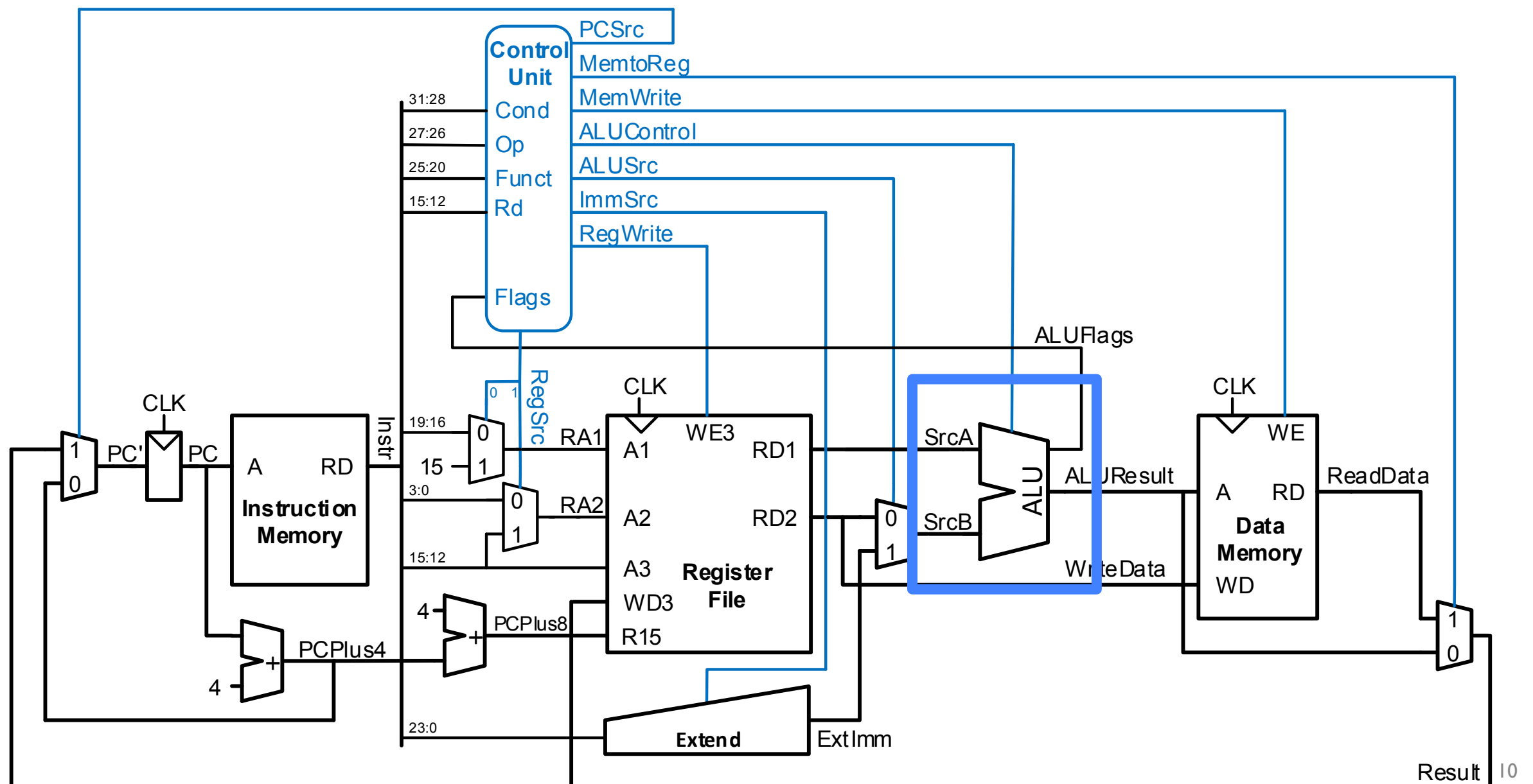
# Arithmetic/Logical Unit


- ALU is one of the main components in the microprocessor.



# ALU: Arithmetic/Logical Unit

- An Arithmetic/Logical Unit (ALU ) combines a variety of **mathematical** and **logical** operations **into a single unit**.
- The ALU forms the heart of most computer systems.


ALUControl <sub>1:0</sub>	Function
00	Add
01	Subtract
10	AND
11	OR

 

The ALU receives a 2-bit **control signal** *ALUControl* that specifies which function to perform.

# ALU Implementation

ALUControl <sub>1:0</sub>	Function
00	Add
01	Subtract
10	AND
11	OR

 

# ALU Implementation


ALUControl <sub>1:0</sub>	Function
00	Add
01	Subtract
10	AND
11	OR

**Example: Perform A OR B**

$ALUControl_{1:0} = 11$

Mux selects output of OR gate as *Result*

***Result = A OR B***

 

# ALU Implementation

ALUControl <sub>1:0</sub>	Function
00	Add
01	Subtract
10	AND
11	OR

## Example: Perform $A + B$


$ALUControl_{1:0} = 00$

$C_{in}$  to adder = 0

2<sup>nd</sup> input to adder is  $B$


Mux selects *Sum* as *Result*

**$Result = A + B$**

 


# ALU with Status Flags

Flag	Description
<i>N</i>	Result is <b>N</b> egative
<i>Z</i>	Result is <b>Z</b> ero
<i>C</i>	Adder produces <b>C</b> arry out
<i>V</i>	Adder o <b>V</b> erflowed

 

Some ALUs produce extra outputs, called **flags**, that indicate information about the ALU output.

# ALU with Status Flags

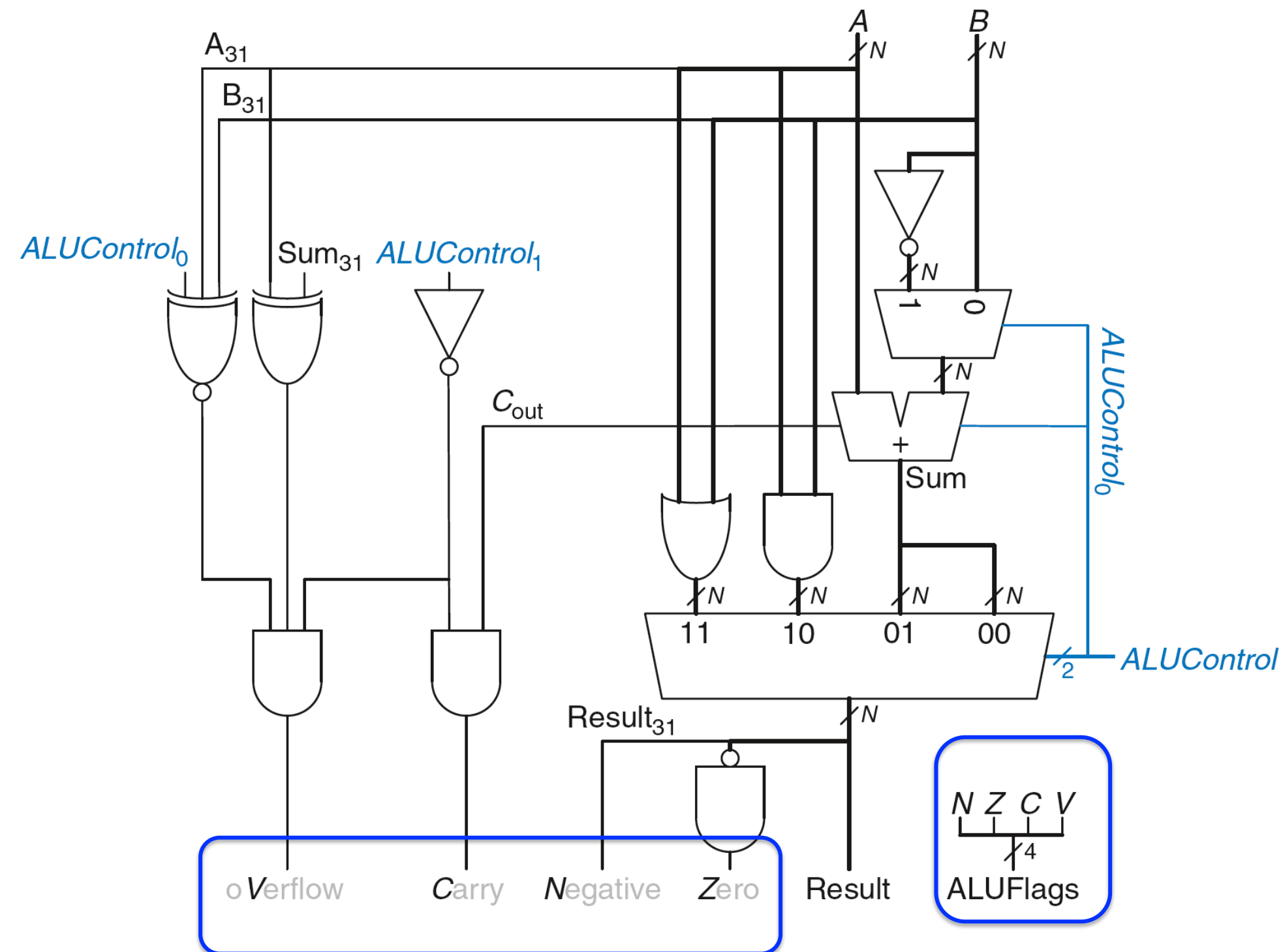




# ALU with Status Flags: **N**egative


**N** = 1 if:

*Result* is **negative**

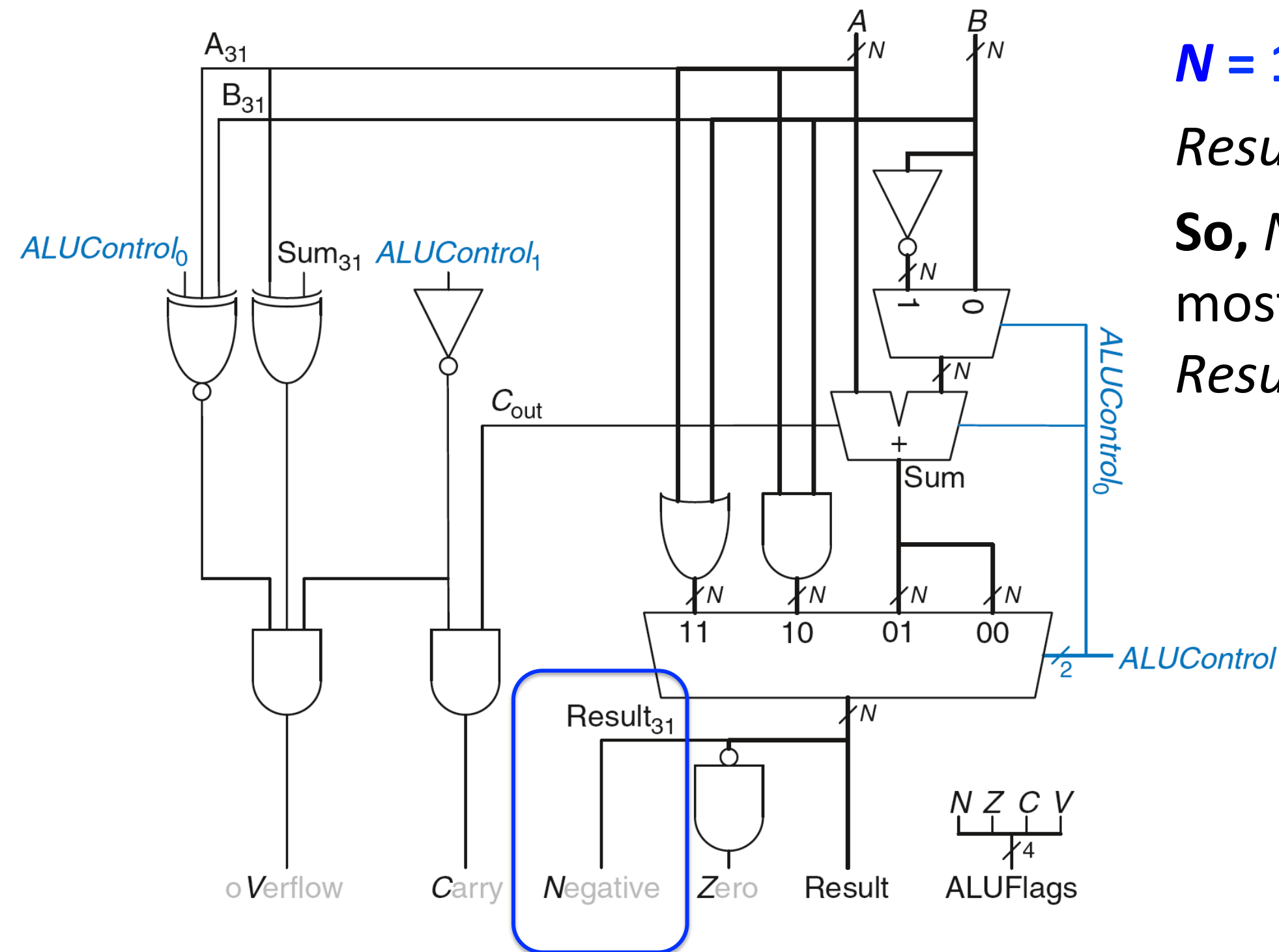**So, N** is connected to  
most significant bit of  
*Result*




# ALU with Status Flags: **Z**ero

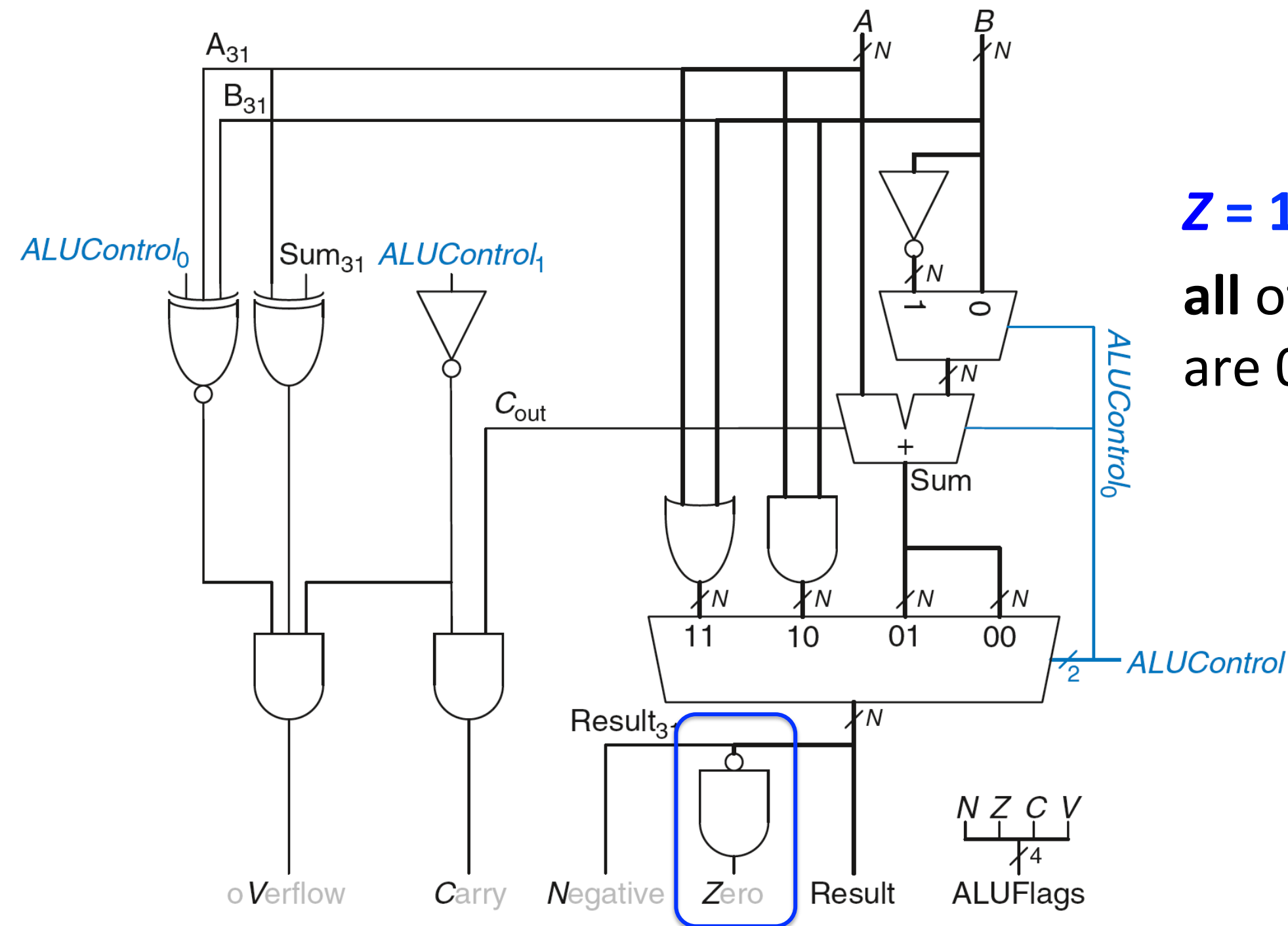

**Z = 1** if:

all of the bits of *Result* are 0

# ALU with Status Flags: Carry

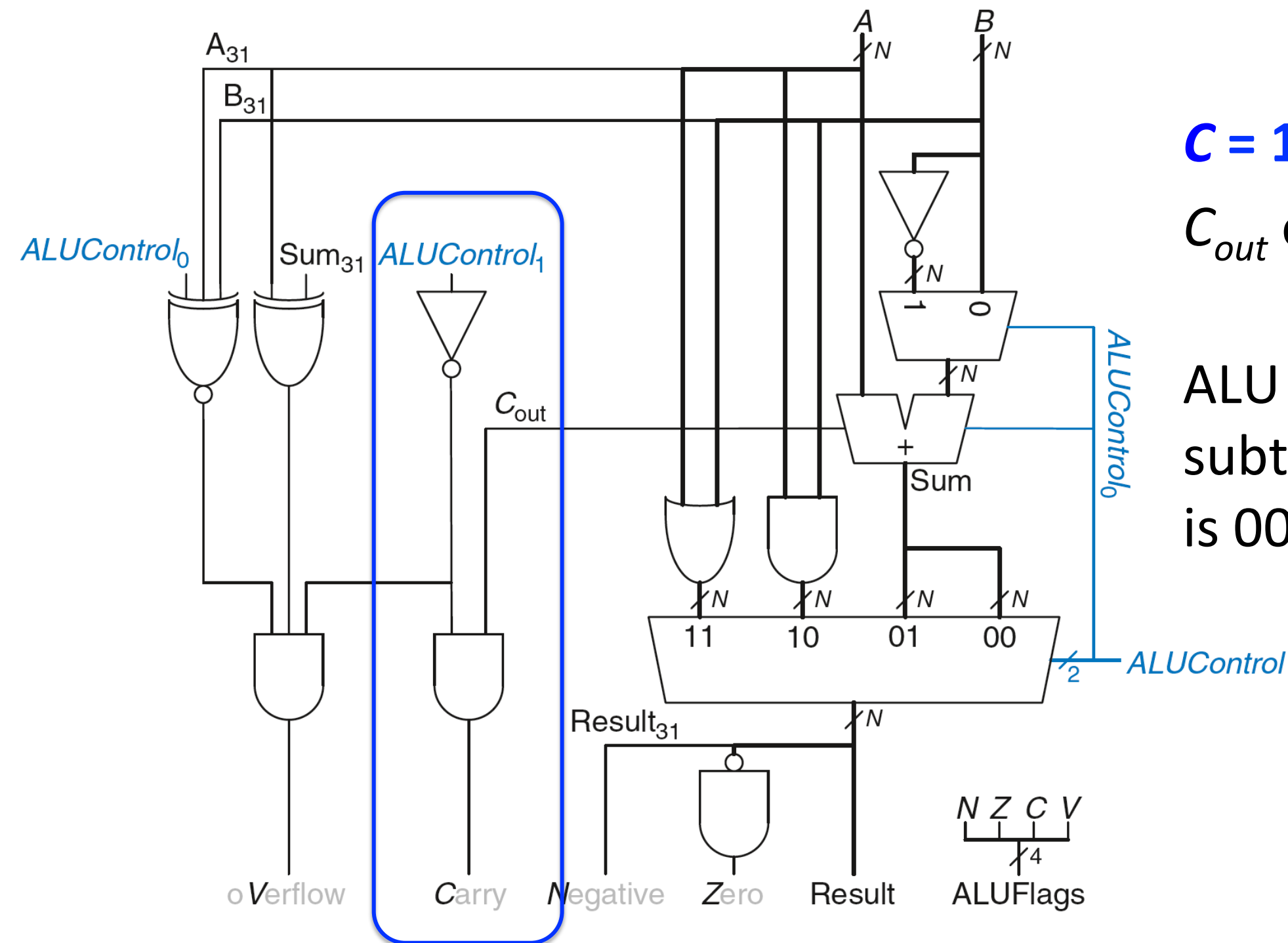


**$C = 1$**  if:

$C_{out}$  of Adder is 1  
**AND**

ALU is adding or  
subtracting ( $ALUControl$   
is 00 or 01)


# ALU with Status Flags: o**V**erflow

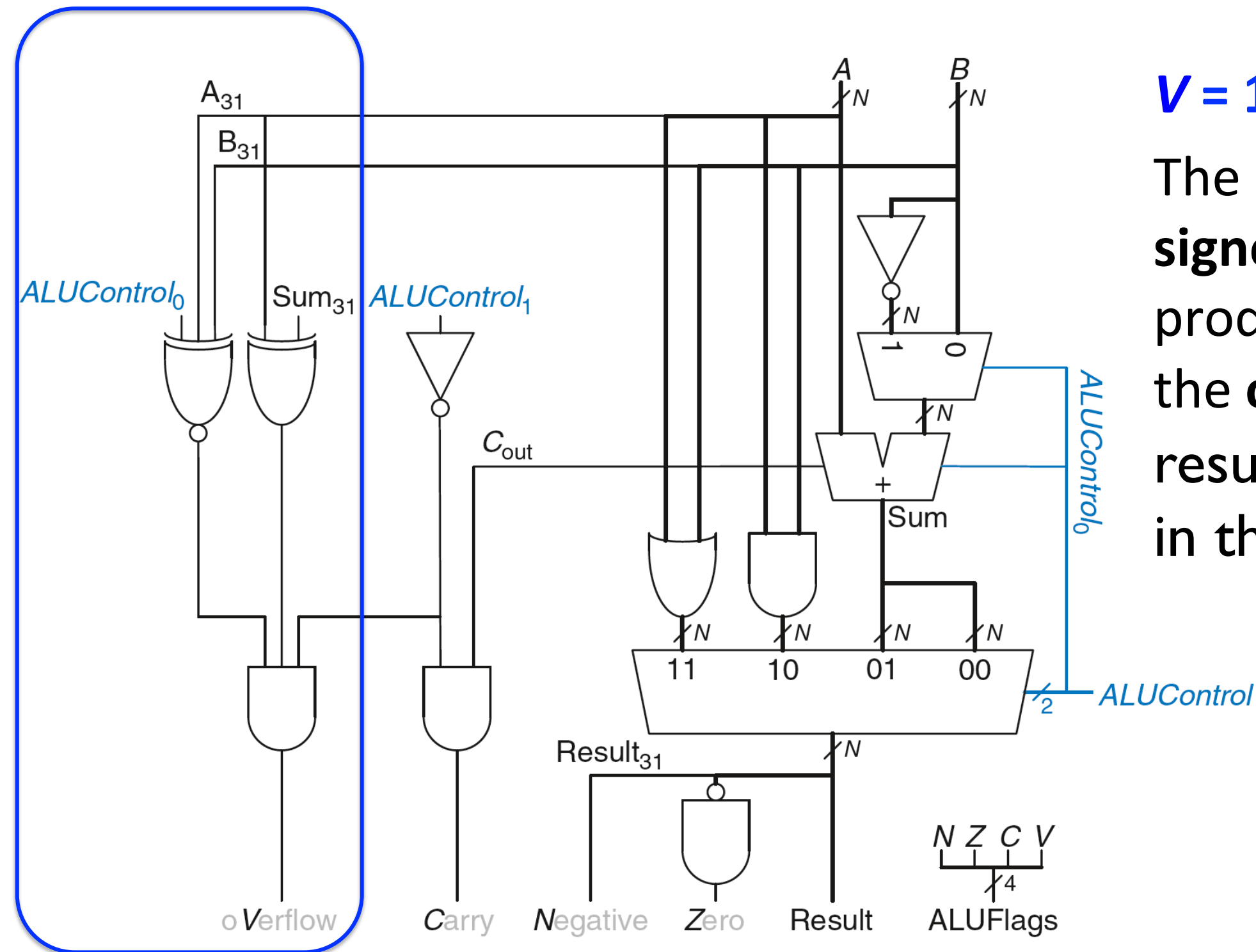

**$V = 1$**  if:

The addition of 2 **same-signed numbers** produces a result with the **opposite sign**. (the result is too big to fit in the available digits.)

# ALU with Status Flags: o**V**erflow

 


**$V = 1$**  if:

ALU is performing addition or subtraction

( **$\text{ALUControl}_1 = 0$** )

# ALU with Status Flags: o**V**erflow

 


**$V = 1$**  if:

ALU is performing addition or subtraction  
( $ALUControl_1 = 0$ )

**AND**

A and Sum have opposite signs

# ALU with Status Flags: o**V**erflow

 

**$V = 1$**  if:

ALU is performing addition or subtraction  
( $ALUControl_1 = 0$ )

**AND**

A and Sum have opposite signs

**AND**

A and B have same signs upon addition  
( $ALUControl_0 = 0$ )

**OR**

A and B have different signs upon subtraction  
( $ALUControl_0 = 1$ )

# Shifters/Rotators

- Shifters and rotators move bits and multiply or divide by powers of 2.
- As the name implies, a shifter **shifts** a binary number left or right by a specified number of positions.

**Logical shifter:** shifts value to left or right and **fills empty spaces with 0's**

—Ex: **11001** >> 2 = 00**110**

—Ex: **11001** << 2 = **001**00



# Shifters/Rotators

**Arithmetic shifter:** right shift, fills empty spaces with the **old most significant bit** (msb)

—Ex: **11**001 >>> 2 = 11**11**0

—Ex: **11**001 <<< 2 = **00**100


**Rotator:** rotates bits in a circle, such that bits shifted off one end are shifted into the other end

—Ex: **11**001 ROR 2 = 01**11**0


—Ex: 11**00**1 ROL 2 = **00**111
 
# Example: Logical Shift Right Implementation

- An **N-bit shifter** can be built from N N:1 multiplexers.
- The input is shifted by 0 to N-1 bits, depending on the value of the  $\log_2 N$ -bit select lines.



 Depending on the value of the 2-bit shift amount  $shamt_{1:0}$ , the output Y receives the input A shifted by 0 to 3 bits.



# Further Reading

- You can read **Chapter 5** of your book
  - **From Section 5.1 to 5.2.5**

