

**EGE UNIVERSITY**  
**LOGIC DESIGN LABORATORY**  
**EXPERIMENT-6**

---

**Sequential Circuit Analysis**

---

**EXPERIMENTAL WORK**

1- Draw the logic diagram for the following system:

$$D_A = Q_A' Q_B + Q_B' X$$


$$D_B = Q_A X$$

$$Z = Q_A Q_B X$$

2- Obtain the **state table** and **state diagram** for the system.

3- **Connect** the circuit and check its operation. Connect  $Q_A$ ,  $Q_B$  and  $Z$  to leds. Use switch for the  $X$  input.

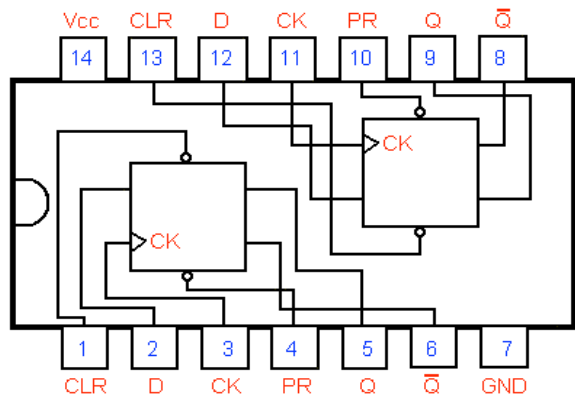**Required Equipment:** 74LS74 Dual Positive-edge Triggered D Flip-flops, 7408 AND, 7432 OR and 7404 NOT gates.



**7474 Dual Positive Edge Triggered D Flip-Flop**

## Function Table

Inputs				Outputs	
PR	CLR	CLK	D	Q	$\bar{Q}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H (Note 1)	H (Note 1)
H	H	$\uparrow$	H	H	L
H	H	$\uparrow$	L	L	H
H	H	L	X	$Q_0$	$\bar{Q}_0$


H = HIGH Logic Level

X = Either LOW or HIGH Logic Level


L = LOW Logic Level

$\uparrow$  = Positive-going Transition

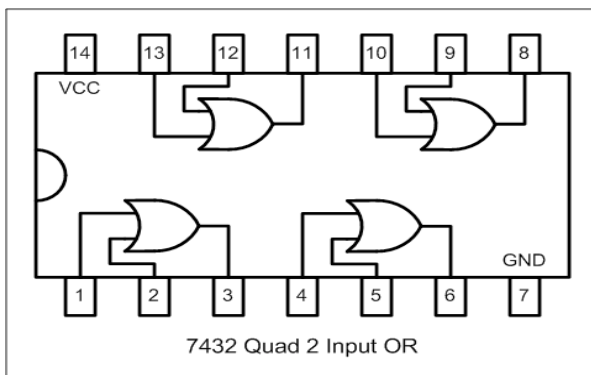
$Q_0$  = The output logic level of Q before the indicated input conditions were established.



**7432 Quad 2 Input OR**

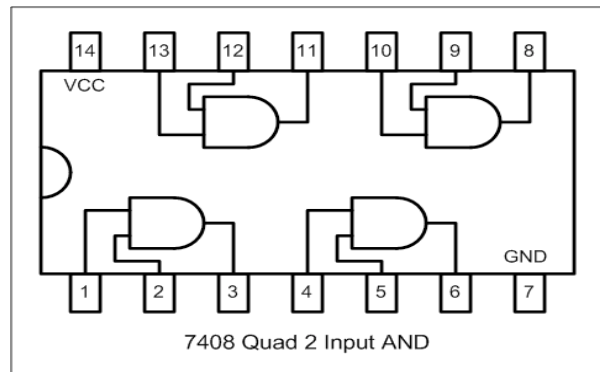

**7408 Quad 2 Input AND**

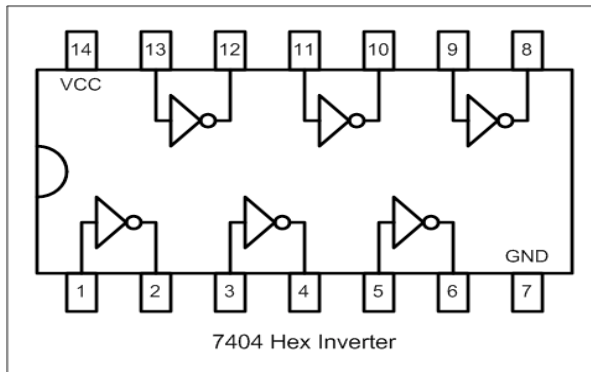

**7404 Hex Inverter**