

Logic Design – Homework 6

- (1)** Design a 4-to-16 decoder using 2-to-4 decoders with enable input.
- (2)** Using four 3x8 decoders with enable input and one 2x4 decoder, design a 5x32 decoder.