

**EGE UNIVERSITY**  
**LOGIC DESIGN LABORATORY**  
**EXPERIMENT-3**

---

**Combinational Circuit Design**

---

**EXPERIMENTAL WORK**

Design a combinational circuit that accepts 4-bit number (ABCD) and generates 3-bit binary number output (XYZ) that approximates the square root of the number. (*For example, if the square root is 3.5 or larger, give the result of 4. If the square root is  $<3.5$  and  $\geq 2.5$ , give a result of 3.*)

1- Fill the truth table and obtain the boolean functions for X, Y and Z outputs using Karnaugh maps.

**TRUTH TABLE**

Inputs				Outputs		
A	B	C	D	X	Y	Z

**KARNAUGH MAP OPTIMIZATION**


X=


Y=


Z=

2- Draw the logic circuit diagram of the Boolean functions X, Y and Z

3- Implement these functions using 7408 AND, 7432 OR and 7404 NOT gates. Use switches for the inputs and connect the outputs to a led.

