


# **HDLs and SystemVerilog**

Digital Computer Design

# Logic Arrays

- Gates can be organized into regular arrays.
  - If the connections are made programmable, these logic arrays can be configured to perform any function without the user having to connect wires in specific ways.
- **Software tools** allow users to map logic designs onto these arrays.
- Two types of logic arrays:
  - programmable logic arrays (PLAs)
  - field programmable gate arrays (FPGAs)

# A FPGA Board

 

# FPGA: Field Programmable Gate Array

FPGA is a reconfigurable substrate

- Reconfigurable functions


- Reconfigurable interconnection of functions

- Reconfigurable input/output (IO)

FPGAs fill the gap between software and hardware

- Achieves higher performance than software

 - Maintains more flexibility than hardware




# LE: Logic Element

- Composed of:
  - **LUTs** (lookup tables): perform combinational logic
  - **Flip-flops**: perform sequential logic
  - **Multiplexers**: connect LUTs and flip-flops

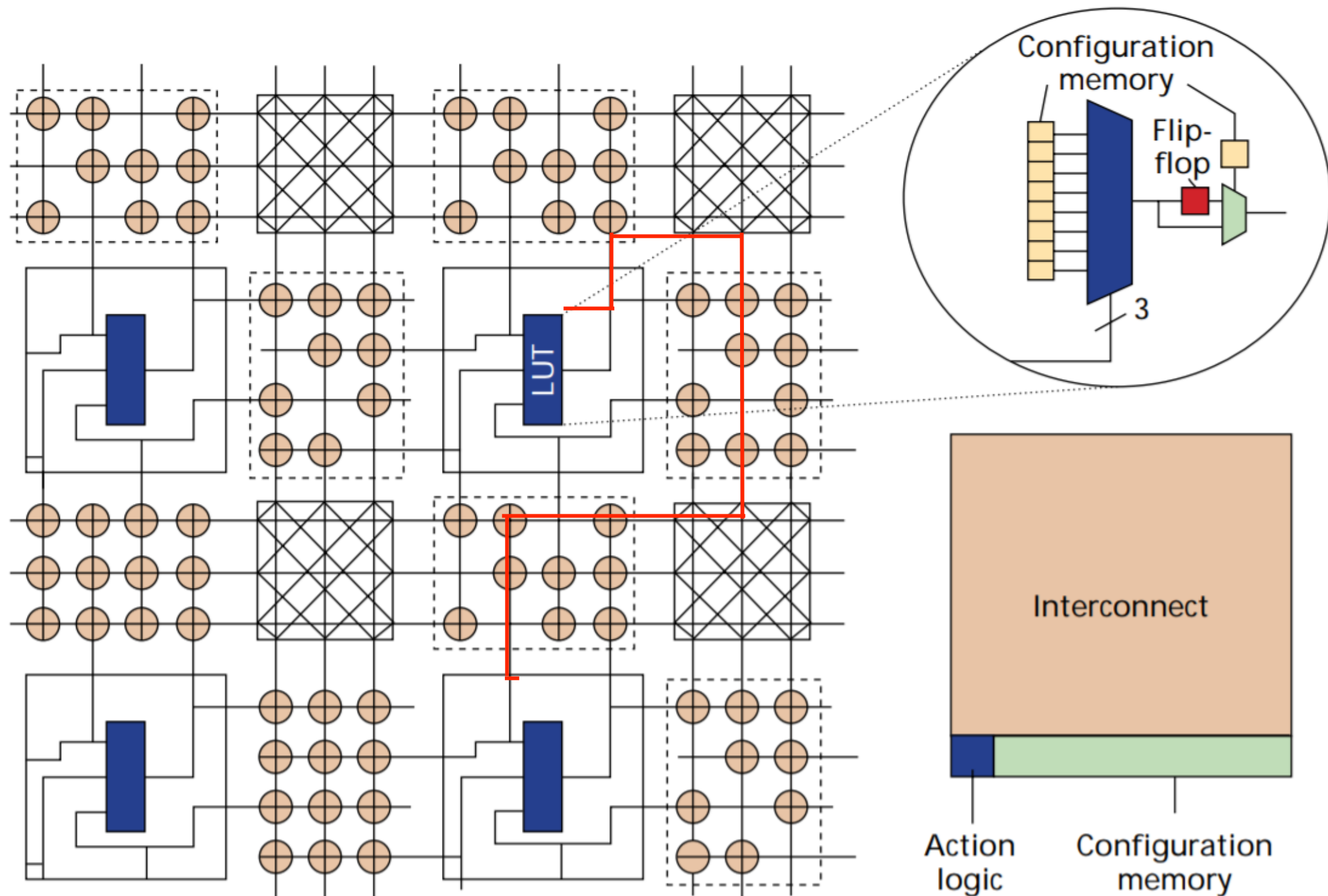
# FPGA Architecture - Looking Inside an FPGA

- Two main building blocks:
  - Look-Up Tables (LUT) and Switches



# How Do We Program LUTs?


- 3-bit input LUT (3-LUT)

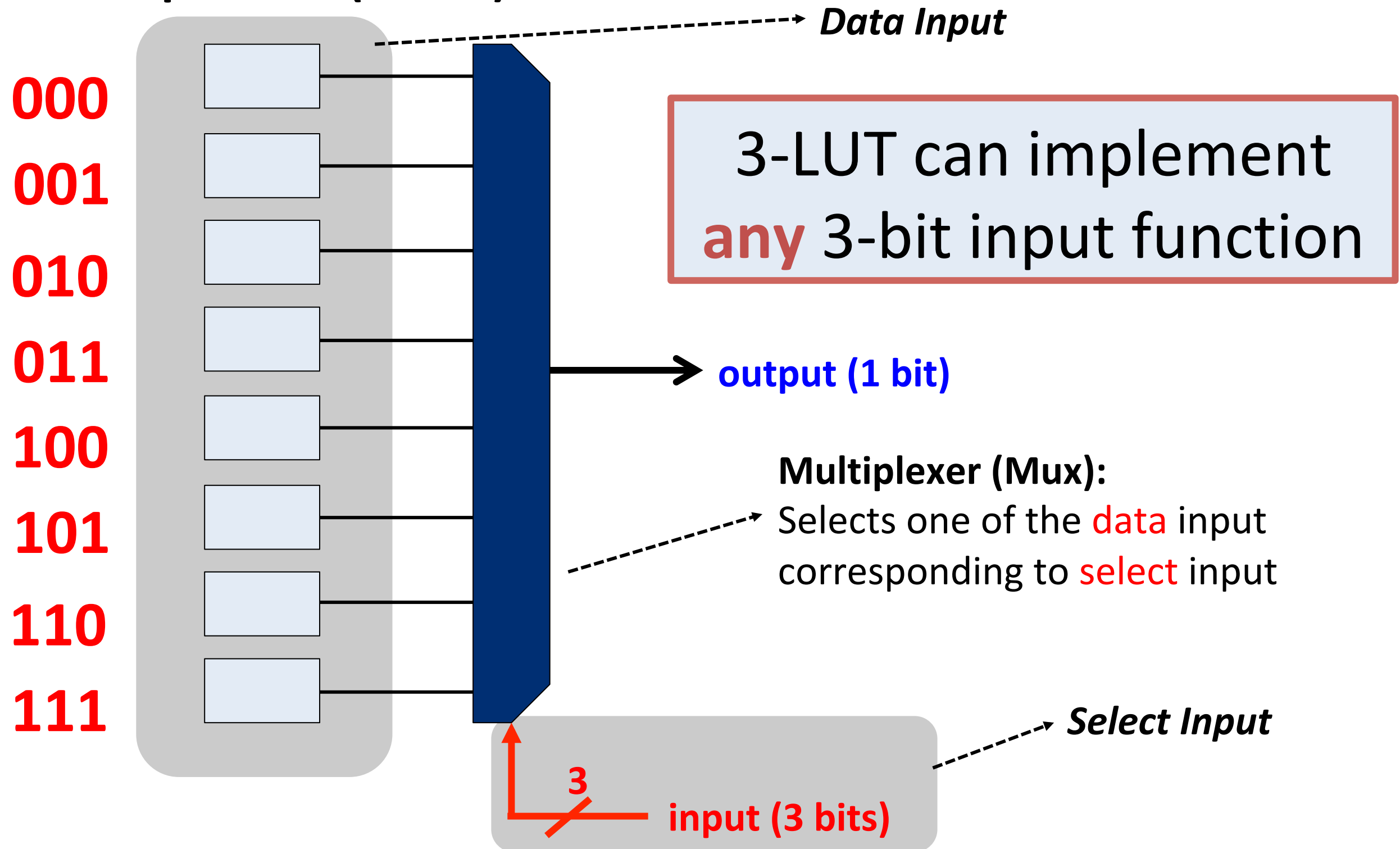


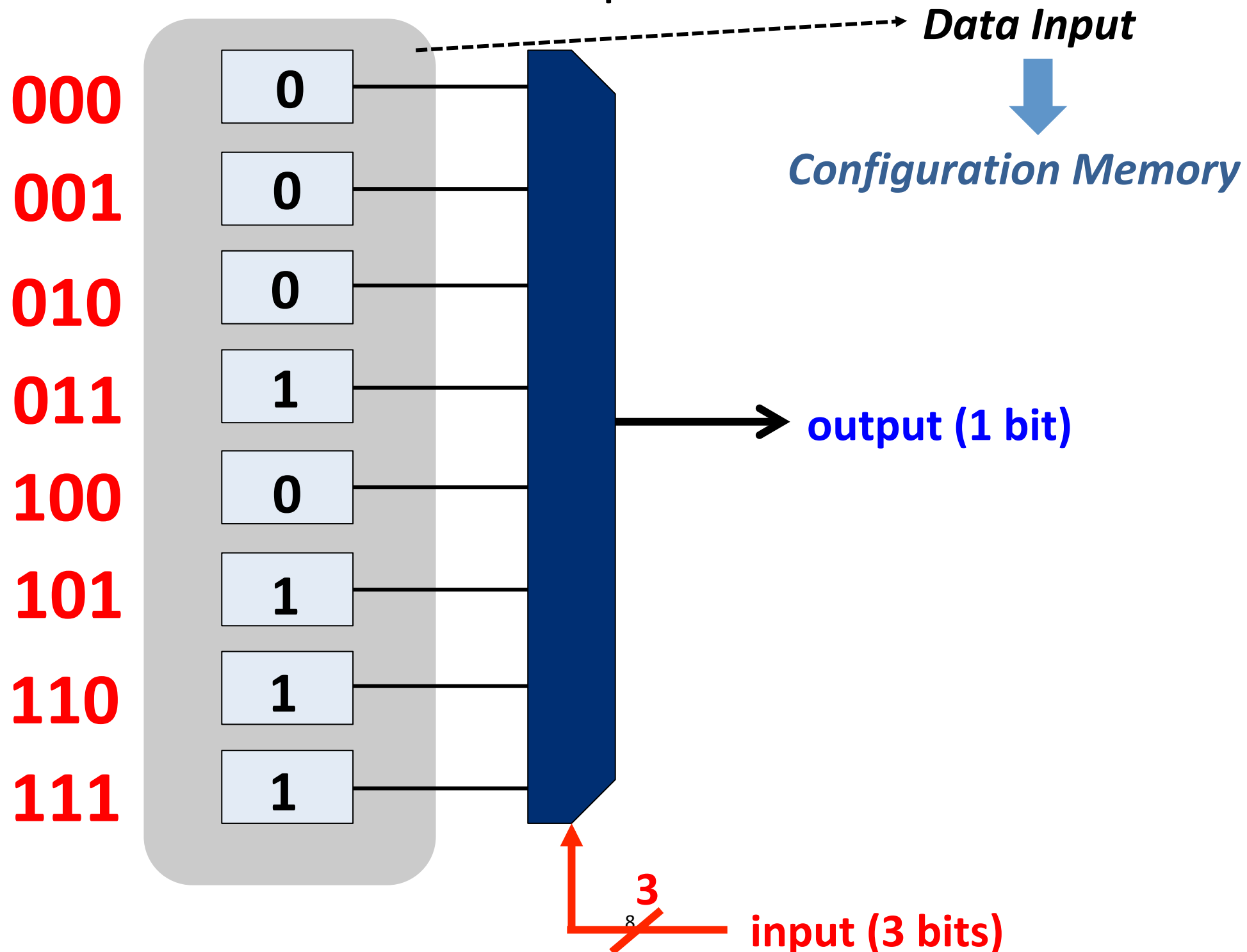
# An Example of Programming a LUT

- Let's implement a function that outputs '1' when there are more than one '1' in select inputs






# How to Implement Complex Functions?

- FPGAs are composed of a large number of LUTs and switches

## FPGA Chip

 

# Advantages & Disadvantages of FPGAs

- Advantages

- Low development cost
- Short time to market
- Reconfigurable in the field
- Reusability
- An algorithm can be implemented directly in hardware
  - No ISA, high specialization

- Disadvantages

- Not as fast and power efficient as *application specific hardware*
- Reconfigurability adds significant area overhead

# Computer-Aided Design (CAD) Tools

FPGAs have many **resources** (e.g., LUTs, switches)

They are **hard** to program manually

How can we


- represent a **high-level functional description** of our hardware circuit using the FPGA resources?

- select the resources to **map** our circuit to?

- optimally configure the interconnect** between the selected resources?

- generate a final **configuration file** to properly configure an FPGA?

# FPGA Design Flow

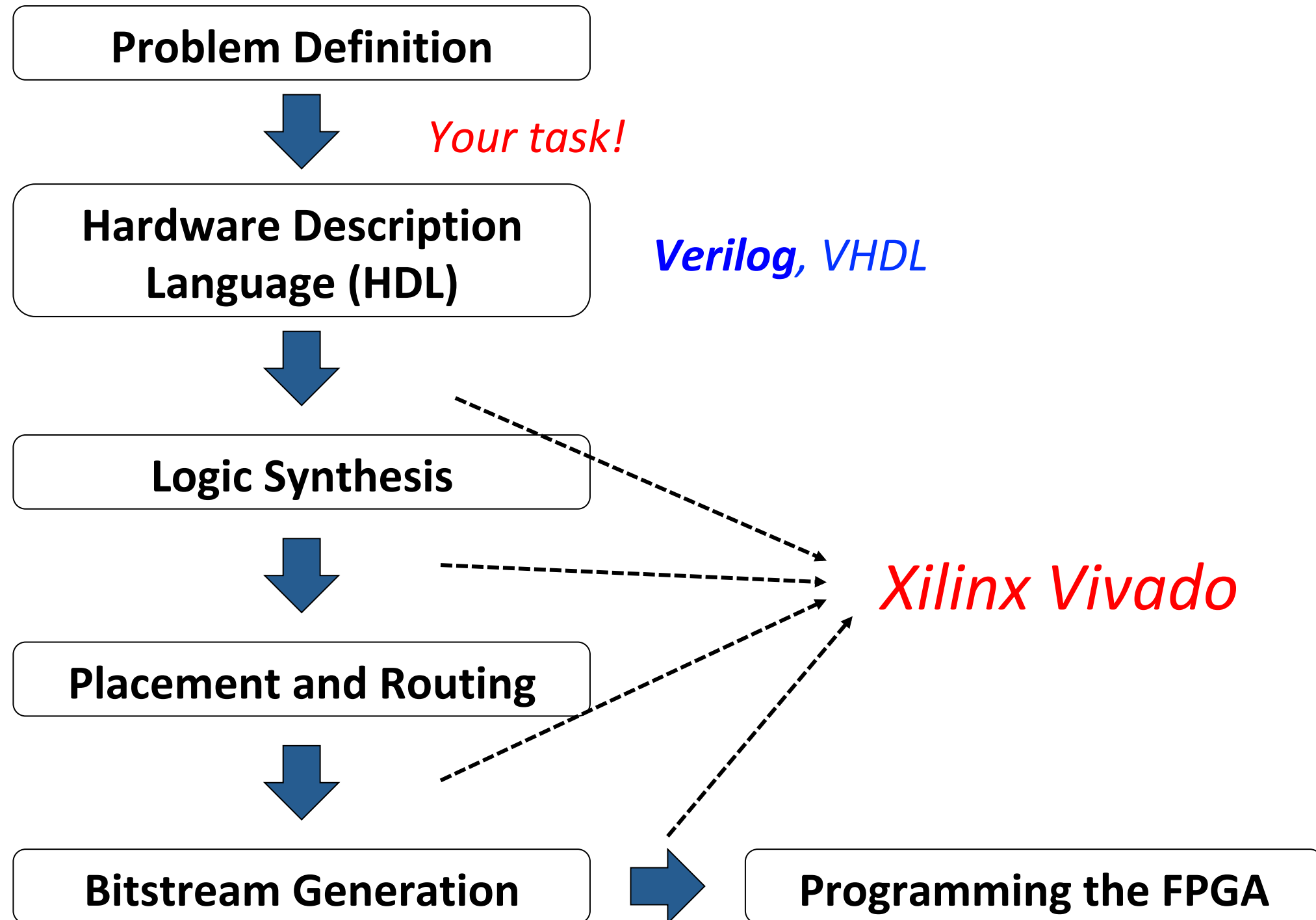

# Hardware description language (HDL)

- Specifies logic function only
  - Computer-aided design (CAD) tool produces or *synthesizes* the optimized gates
  - Think of the **hardware** the HDL should produce!
- Most commercial designs built using HDLs
- Two leading HDLs:
  - **SystemVerilog**
    - developed in 1984 by Gateway Design Automation
    - IEEE standard (1364) in 1995
    - Extended in 2005 (IEEE STD 1800-2009)
  - **VHDL 2008**
    - Developed in 1981 by the Department of Defense
    - IEEE standard (1076) in 1987
    - Updated in 2008 (IEEE STD 1076-2008)

# HDL to Gates

- **Simulation**


- Inputs applied to circuit
- Outputs checked for correctness
- Millions of dollars saved by debugging in simulation instead of hardware

- **Synthesis**

- Transforms HDL code into a *netlist* describing the hardware (i.e., a list of gates and the wires connecting them)
 
# SystemVerilog Modules

- A block of hardware with inputs and outputs is called a module.
- **Two types of Modules:**
  - **Behavioral:** describe what a module does
  - **Structural:** describe how it is built from simpler modules






# Behavioral SystemVerilog

- **module/endmodule**: required to begin/end module
- **example**: name of the module
- Operators:
  - ~: NOT
  - &: AND
  - |: OR

```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a  
               & ~b & c;  
endmodule
```

# HDL Simulation


```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a  
              & ~b & c;  
endmodule
```

 

Inputs applied to circuit, Outputs checked for correctness

# HDL Synthesis

```
module example(input  logic a, b, c,  
               output logic y);  
    assign y = ~a & ~b & ~c | a & ~b & ~c | a  
              & ~b & c;  
endmodule
```

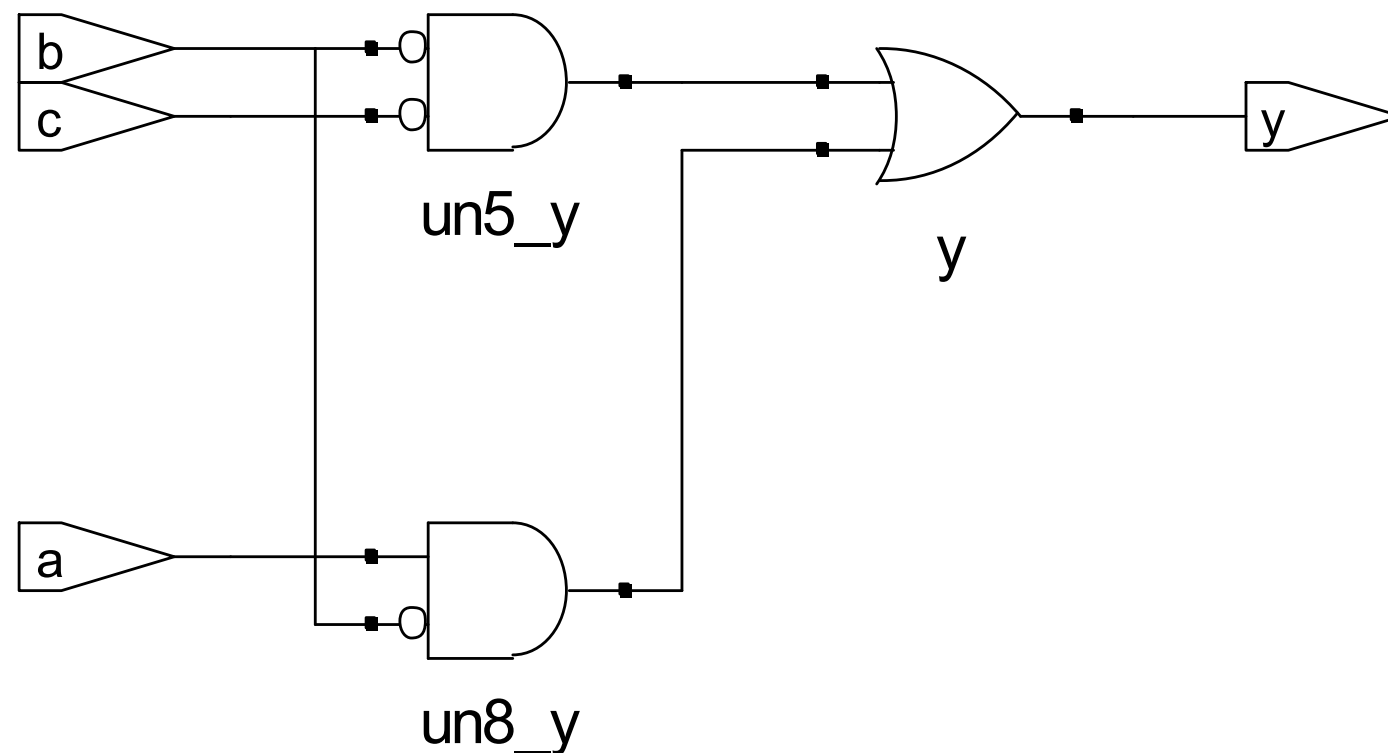

Transforms HDL code into a **netlist** describing the hardware (i.e., a list of gates and the wires connecting them)

# Further Reading

- You can read **Chapter 4** of your book.

