

Logic Design – Homework 5

(1) Design the following combinational circuits.

- (a) Takes 3-bit input and outputs the 3-bit complement of the input.
- (b) Takes 3-bit input and outputs 1 when the number of 1's in the input number is smaller than the number of 0's.
- (c) Takes 3-bit input such that when the input is 0,1,2,3 then the output is plus 1 and in other cases minus 1 of the input.
- (d) Takes a BCD number as an input and outputs 3 times of the input in BCD form.
- (e) Takes 3-bit input and outputs its square.
- (f) Takes 4-bit input and outputs the 2's complement of the input.
- (g) Takes BCD input and outputs 1 if the top led of the 7-segment display is on.
- (h) Takes 4-bit input and outputs 1 if the input is not BCD.
- (i) Takes 3-bit input and determines the number of 1's in it.

(2) Implement the following circuits with only

- (a) 2-input NAND
 - (b) 2-input NOR
- gates and inverters.

$$F = W(X+Y+Z)+XYZ$$

$$F = ab'c' + b(c'+d')$$

$$F = X+Y (Z+ X+Z)$$