

EGE UNIVERSITY
LOGIC DESIGN LABORATORY
EXPERIMENT-7

Sequential Circuit Analysis

EXPERIMENTAL WORK

1- Draw the logic diagram for the following system:

$$D_A = Q_A' Q_B + Q_B' X$$


$$D_B = Q_A X$$

$$Z = Q_A Q_B X$$

2- Obtain the **state table** and **state diagram** for the system.

3- **Connect** the circuit and check its operation. Connect Q_A , Q_B and Z to leds. Use switch for the X input.

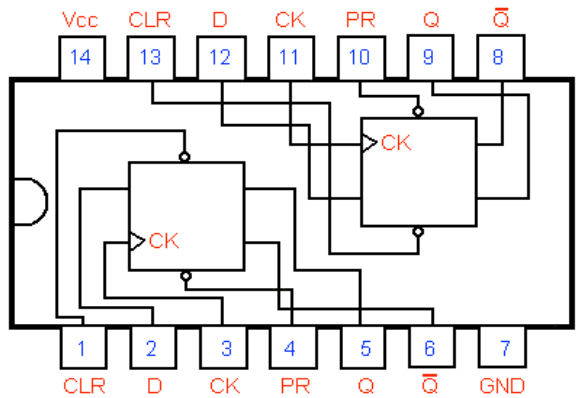Required Equipment: **74LS74** Dual Positive-edge Triggered D Flip-flops, **7408** AND, **7432** OR and **7404** NOT gates.



7474 Dual Positive Edge Triggered D Flip-Flop

Function Table

Inputs				Outputs	
PR	CLR	CLK	D	Q	\bar{Q}
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H (Note 1)	H (Note 1)
H	H	\uparrow	H	H	L
H	H	\uparrow	L	L	H
H	H	L	X	Q_0	\bar{Q}_0


H = HIGH Logic Level

X = Either LOW or HIGH Logic Level


L = LOW Logic Level

\uparrow = Positive-going Transition

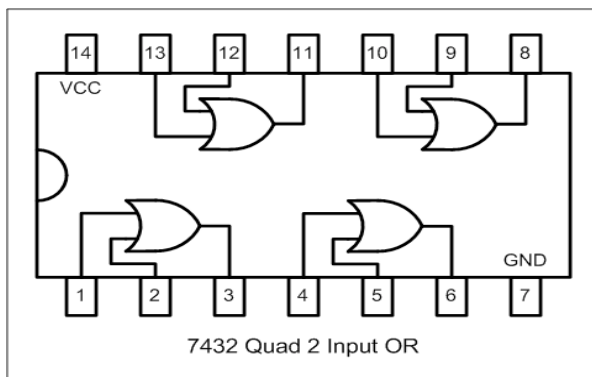
Q_0 = The output logic level of Q before the indicated input conditions were established.



7432 Quad 2 Input OR

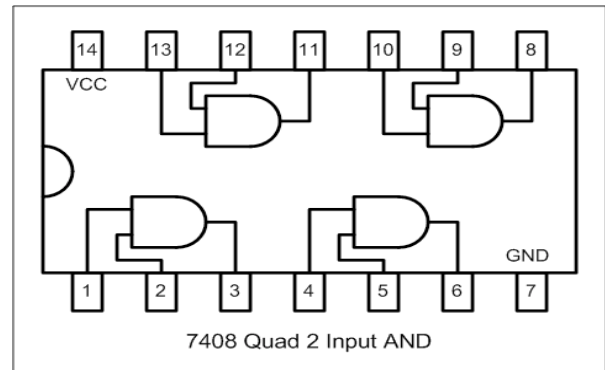

7408 Quad 2 Input AND

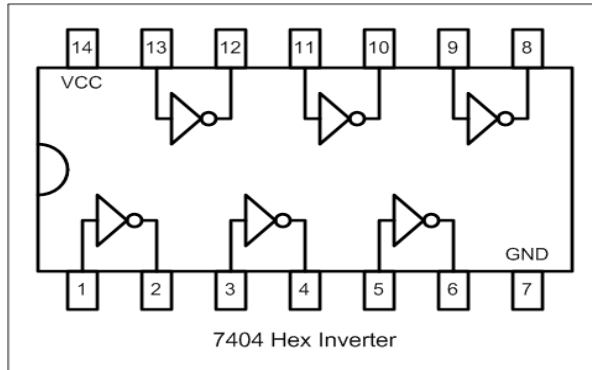

7404 Hex Inverter