

Logic Design – Homework 4

(1) Draw the logic diagram for the following Boolean expressions:

(a) $XYZ' + XY' + X'Z$

(b) $X + X'(X' + Y) + (Y' + Z)$

(2) Prove the identity of each of the following Boolean equations using algebraic manipulation.

(a) $X'Y' + X'Y + XY = X' + Y$

(b) $A'B + B'C' + AB + B'C = 1$

(c) $Y + X'Z + XY' = X + Y + Z$

(3) Simplify the following expressions by using Boolean algebra.

(a) $F = (X(Y' + V + X'))' + ((X + Z' + W')(Y + V + W'))'$

(b) $F = X + Y(Z + (X + Z)')$

(c) $F = WX(Z + YZ) + X(W + WYZ)$

(4) Using DeMorgan's theorem, express the function $F = A'BC + AC' + A'B$

(a) with only OR and complement operations

(b) with only AND and complement operations

(5) Express the following functions in sum of minterms and product of maxterms forms.

(a) $F(X, Y, Z) = (X + YZ)(Z + YX)$

(b) $F(XYZ) = X' + X(X + Y')(Y'Z')$